

Code No: X0224

**R07****SET - 1**

**II B. Tech I Semester Supplementary Examinations May – 2013**  
**SWITCHING THEORY AND LOGIC DESIGN**

(Com. to EEE, EIE, BME, ECC)

Time: 3 hours

Max. Marks: 80

Answer any **FIVE** Questions  
 All Questions carry **Equal** Marks

~~~~~

1. a) How to convert a gray number to binary? Explain with the help of suitable examples?  
 b) Perform the following binary subtraction:  
     i) 1011-101    ii) 10110-1011    iii) 1100.10-111.01    iv) 10001.01-1111.11  
 c) Convert the following numbers into the gray numbers  
     i)  $3A7_{16}$     ii)  $527_8$     iii)  $652_{10}$
  
2. a) Name the gates that are used as universal gates? Explain?  
 b) Realize the following function as i) Multilevel NAND-NAND gate network    ii) Multilevel NOR-NOR network.  

$$f = B(A + CD) + A\bar{C}$$
  
3. a) Simplify the Boolean function using SOP.  
     i)  $f(A, B, C, D) = \sum (0, 1, 2, 5, 8, 9, 10)$   
     ii)  $f(A, B, C, D) = \sum (0, 1, 2, 3, 7, 8, 9, 10, 11, 12, 13)$   
 b) Reduce the following expressions using K-maps  
     i)  $AB + \bar{A}BC + \bar{A}\bar{B}C + BC$   
     ii)  $ABC + AB + C + \bar{B}C + D\bar{B}$
  
4. a) Design a 32:1 multiplexer using two 16:1 and 2:1 multiplexers.  
 b) Realize the logic expressions given below using a  
     i) 8:1 MUX    ii) 16:1 MUX  

$$F = \sum_m (0, 1, 3, 5, 8, 11, 12, 14, 15)$$
  
5. a) Compare the three combinational PLDs-PROM, PLA and PAL.  
 b) Tabulate the PLA programming table for the four Boolean functions listed below  

$$A(x,y,z) = \varepsilon (1, 2, 4, 6)$$

$$B(x,y,z) = \varepsilon (0, 1, 6, 7)$$

$$C(x,y,z) = \varepsilon (2,6)$$

$$D(x,y,z) = \varepsilon (1, 2, 3, 5, 7)$$

Code No: X0224

**R07****SET - 1**

6. a) Distinguish between combinational and sequential switching circuits?  
 b) What are the various methods used for triggering a flip-flop?  
 c) Design a sequence detector which generates an output  $z=1$ , whenever the string is 0110 and generates a 0 at all other times. The overlapping sequences are detected. Implement the circuit using D flip flops.
7. a) Compare and contrast the Moore machine and the Melay machine.  
 b) Obtain the set of maximal compatibles for the sequential machine whose state table is shown in the following table, by using the merger table method.

| PS | NS, Z          |                |                |                |
|----|----------------|----------------|----------------|----------------|
|    | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> | I <sub>4</sub> |
| A  | -              | C,1            | E,1            | B,1            |
| B  | E,0            | -              | -              | -              |
| C  | F,0            | F,1            | -              | -              |
| D  | -              | -              | B,1            | -              |
| E  | -              | F,1            | A,0            | D,1            |
| F  | C,0            | -              | B,0            | C,1            |

8. Obtain the ASM chart for the following state transitions:  
 a) If  $x=0$ , control goes from state  $T_1$  to state  $T_2$ . If  $x=1$ , generate the conditional operation and go from  $T_1$  to  $T_2$ .  
 b) If  $x=1$ , control goes from  $T_1$  to  $T_2$  and then to  $T_3$ . If  $x=0$ , control goes from  $T_1$  to  $T_3$

Code No: X0224

**R07****SET - 2****II B. Tech I Semester Supplementary Examinations May – 2013****SWITCHING THEORY AND LOGIC DESIGN**

(Com. to EEE, EIE, BME, ECC)

Time: 3 hours

Max. Marks: 80

Answer any **FIVE** Questions  
All Questions carry **Equal** Marks

~~~~~

1. a) What do you mean by an error correcting code?  
b) Perform the following subtractions in excess-3 code using the 9's complement method.  
i) 687-348                      ii) 246-592  
c) Convert the following numbers with the given radix to decimal and binary.  
i) 4433<sub>5</sub>                      ii) 1199<sub>12</sub>                      iii) 5654<sub>7</sub>
2. a) Explain how the basic gates can be realized using NAND gates.  
b) Realize i)  $Y = A + B\overline{C\overline{D}}$  using NAND gates and ii)  $Y = (A + C)(A + \overline{D})(A + B + \overline{C})$  using NOR gates.  
c) Reduce the following Boolean expressions  
i)  $AB + BB + C + \overline{B}$                       ii)  $(AB + C)(AB + D)$
3. Obtain the minimal expression using the tabular method and implement it in universal logic.  
 $\sum_m (1, 5, 6, 12, 13, 14) + d(2, 4)$
4. a) Design a circuit to convert excess-3 code into BCD code using a 4 bit full adder.  
b) Implement the function  $F(a, b, c, d) = a\overline{b} + acd + b\overline{c} + d$  using a MUX with 3 select inputs.
5. Write a short note on the following  
a) Architecture of PLDs  
b) Capabilities and limitations of threshold gates
6. a) Define the following terms with relation to flip-flops  
i) Set-up time                      ii) hold time                      iii) propagation delay time  
iv) Preset                      v) clear.  
b) Draw the circuit diagram of 4-bit ring counter using D-flip flops and explain its operation  
With the help of bit pattern.

Code No: X0224

**R07****SET - 2**

7. a) Explain the limitations of finite state machines.  
 b) Find the equivalence partition and a corresponding reduced machine in standard form for the machine given in table

PS	NS,Z	
	X=0	X=1
A	E,0	D,1
B	F,0	D,0
C	E,0	B,1
D	F,0	B,0
E	C,0	F,1
F	B,0	C,0

8. a) List out the salient features of ASM charts.  
 b) Draw the ASM chart for the following state transition, start from the initial state  $T_1$ , then if  $xy=00$  go to  $T_2$ , if  $xy=01$  go to  $T_3$ , if  $xy=10$  go to  $T_1$ , otherwise go to  $T_3$  and design its control circuit using D-flip flop and decoder.

Code No: X0224

**R07****SET - 3**

**II B. Tech I Semester Supplementary Examinations May – 2013**  
**SWITCHING THEORY AND LOGIC DESIGN**

(Com. to EEE, EIE, BME, ECC)

Time: 3 hours

Max. Marks: 80

Answer any **FIVE** Questions  
 All Questions carry **Equal** Marks

~~~~~

- What is the Hamming code? How is the Hamming code word tested and corrected?
  - Explain binary subtraction using the 1's and 2's complement methods.
  - Convert the following decimal numbers to octal numbers and then decimal to binary.
    - 59
    - 64.5
    - 199.3
- What do you mean by the principle of duality? List out the properties of Boolean algebra.
  - Simplify the following expressions
    - $\overline{A}B + C\overline{D}$
    - $AB + \overline{A}C + A\overline{B}C(AB + C)$
    - $(\overline{A} + B)(A + B)$
    - $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC\overline{C}$
- Simplify the Boolean function using SOP.
    - $f(A, B, C, D) = \sum(1, 3, 7, 11, 15) + \sum_d(0, 2, 5)$
    - $f(A, B, C, D) = \sum(1, 2, 5, 6, 9) + \sum_d(10, 11, 12, 13, 14, 15)$
  - Reduce the following expressions using K-maps
    - $(A + B)(A + \overline{B} + C)(A + \overline{C})$
    - $(\overline{A} + B)(A + B + \overline{D})(B + \overline{C})(B + CD)$
- Show how a 16:1 MUX can be realized using 4:1 MUX.
  - Implement the following logic function using an 8:1 MUX  
 $F(a, b, c, d) = \overline{a}b + \overline{c}d + a\overline{c}$
- Derive the PLA programming table for the combinational circuit that squares a 3 bit number.
  - For the given 3-input, 4-output truth table of a combinations circuit, tabulate the PAL programming table for the circuit.

| Inputs |   |   | Output |   |   |   |
|--------|---|---|--------|---|---|---|
| x      | y | z | A      | B | C | D |
| 0      | 0 | 0 | 0      | 1 | 0 | 0 |
| 0      | 0 | 1 | 1      | 1 | 1 | 1 |
| 0      | 1 | 0 | 1      | 0 | 1 | 1 |
| 0      | 1 | 1 | 0      | 1 | 0 | 1 |
| 1      | 0 | 0 | 1      | 0 | 1 | 0 |
| 1      | 0 | 1 | 0      | 0 | 0 | 1 |
| 1      | 1 | 0 | 1      | 1 | 1 | 0 |
| 1      | 1 | 1 | 0      | 1 | 1 | 1 |

1 of 2

Code No: X0224

**R07****SET - 3**

6. a) What is serial binary adder? Explain its working with the help of a state diagram.  
b) Design a Mod-6 synchronous counter using J-K flip flops.
7. a) Distinguish between Mealy and Moore machines  
b) Convert the following Mealy machine into a corresponding Moore machine

| PS | NS,Z |     |
|----|------|-----|
|    | X=0  | X=1 |
| A  | B,0  | E,0 |
| B  | E,0  | D,0 |
| C  | D,1  | A,0 |
| D  | C,1  | E,0 |
| E  | B,0  | D,0 |

8. a) Draw and explain the ASM chart for a weighing machine.  
b) Show the exit paths in an ASM block for all binary combinations of control variables x, y and z, starting from an initial state.

Code No: X0224

**R07**

**SET - 4**

**II B. Tech I Semester Supplementary Examinations May – 2013  
SWITCHING THEORY AND LOGIC DESIGN**

(Com. to EEE, EIE, BME, ECC)

Time: 3 hours

Max. Marks: 80

Answer any **FIVE** Questions  
All Questions carry **Equal** Marks

~~~~~

1. a) List the salient features of the BCD, Excess-3 and Gray codes.  
 b) How do you add two decimal numbers in the BCD form if the sum is greater than 9?  
 c) Multiply the following binary numbers  
     i) 1011 and 1101      ii) 100110 and 1001      iii) 1.01 and 10.1
  
2. a) obtain the duals of the following functions  
     i)  $\overline{A}B + \overline{A}B\overline{C} + \overline{A}BCD + \overline{A}B\overline{C}DE$       ii)  $ABEF + AB\overline{E}\overline{F} + \overline{A}\overline{B}EF$   
     iii)  $\overline{X}Z + \overline{X}Y + X\overline{Y}Z + YZ$       iv)  $AB + \overline{A}C + \overline{A}B\overline{C}$   
 b) Reduce the following Boolean expressions  
     i)  $AB + A(B + C) + \overline{B}(B + D)$       ii)  $(X + Y + Z)(\overline{X} + \overline{Y} + \overline{Z})X$   
     iii)  $A + B + \overline{A}\overline{B}C$       iv)  $X(YZ + \overline{Y}Z)$
  
3. Obtain the minimal expression using the tabular method and implement it in universal logic.  
 $\prod_M (1, 5, 6, 7, 11, 12, 13, 15)$
  
4. a) Write about the hazards and hazard free realizations.  
 b) Design binary to gray code converter.
  
5. Find the function  $f(x_1, x_2, x_3, x_4)$  realized by each of the threshold networks shown in the figure: 5(a) i, 5(a)ii, 5b.

 


Figure 5(a)i

 


Figure 5(a)ii

 


Figure 5b

Code No: X0224

**R07****SET - 4**

6. a) Explain the following
- Race around condition in J-K flip flop
  - Excitation table for flip-flops.
- b) Give the design of 4 bit Ring counter and explain with the help of waveforms. Also give the application of this ring counter.
7. What are the conditions for the two machines to be equivalent? For the machine given below, find the equivalence partition and a corresponding reduced machine in standard form:

PS	NS,Z	
	X=0	X=1
A	F,0	B,1
B	G,0	A,1
C	B,0	C,1
D	C,0	B,1
E	D,0	A,1
F	E,1	F,1
G	E,1	G,1

8. a) Draw and explain the ASM chart for a binary multiplier.
- b) Draw an ASM chart, a state diagram for the synchronous circuit having the following description. The circuit has a control input C, clock and outputs x,y,z.
- If C=1, on every clock rising edge, the code on the output x, y, z changes from 000→010→100→110→000 and repeats.
  - If C=0, the circuit holds the present state.