

www.FirstRanker.com

www.FirstRanker.com

Mettle

USN

1:7ELN15

First Semester B.E. Degree Examination, Dec.2017/Jan.2018 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing one full question from each module.

То	<u>Module-1</u>				
го Ся	a. Explain the operation of FIN junction though the for ward and reverse blased conditions (06 Marks)				
cu	b. Derive the relation between a and 10 . Calculate Ic and IE for transistor that has $ad_{1} = 0.98$				
. 42		~	and $1B = 100$ IAA.	(06 Marks)	
XI O		с.,	With a neat circuit diagram and waveforms, explain the working of centre-tap	full wave	
$\mathbf{L}^{\mathbf{L}}$			rectifier and derive the e fficiency for the same.	(08 Marks)	
			OR		
č∔ 'a' 4	2 a	a.	With a neat diagram, explain the operation of PNP and NPN transistor.	(08 Marks)	
g bb		b.	A half wave rectifier from a supply 230 V 50 Hz with step down transformer rati	o 3:1 to a	
0	—		resistive load of 10 Kn. The diode forward resistance is 75 f2 and transformer see	condary is	
c.r. 0}			10 Q. Calculate the DC current, DC voltage, efficiency and ripple factor.	(06 Marks)	
Our . c		c.	With neat circuit diagrani, e lain•, the common emitter circuit and sketch the	input and	
`,2 tE;			output characteristics.	(06 Marks)	
74 o			Module 2		
- @ []	39	Wi	th a necessary equation and circuit explain the bage-bias transistor circuits	(06 Marks)	
a vi	5 a	 b.	Design an Adder using on-amp to give the output voltage.	(00 Marks)	
			$V_0 = -f2V_1 + 3V_2 + 5V_3$	(06 Marks)	
<u>ک</u> (چ ر		C.	Derive the equations for output voltage for an inverting arianlifier and an integrator.	(*************	
$\frac{cn Ca}{= 0}$			berre the equations for output, orage for an inverting a tupinter and an integrator.	(08 Marks)	
a. ••) σ R					
₿ď			OR		
'52 i2	4	a.	Explain the characteristics of an ideal op-amp. Mention the application&	(06 Marks)	
Ĩ€		b. <i>I</i>	Accurately analyze the voltage divider bias which has $Vcc = 18 V$, RI =	= 33 KK2,	
o '?'			R2 = 12 Ka and $RE = 1$ KO. Determine VE VC, VCE, IC and Q point, when	(08 Marilar)	
0 		С. х	h fe = 200. Nrite shart nates an an-amn virtual ground concent	(06 Marks)	
			white short notes on op-amp virtual ground concept.	(00 Marks)	
u	-		Module-3		
•	5	a. I	erform the following:		
			1) CUIIVEI (3/343)10 — ()16 ii) Subtract (28)10 — (19)10 using 2's complement method	(06 Mark e)	
.8		h	Realize $V = AB + CD + F$ using NAND gate	(06 Marke)	
=		с. F	Explain the full adder circuit with truth table. Realize the circuit for sum and ca	rry using	
i-			logic gates.	(08 Marks)	
				. /	



www.FirstRanker.com

www.FirstRanker.com

17ELN15

OR

6 a Perform the following:

- i) Convert (FA27D)to = ()2 \rightarrow = ()8 = ()to
- ii) Subtract 10.0101 101.1110 using l's compliment method. (06 Marks)
 b. y = A +AB+ ABC simplify and implement using logic gates and NOR gates. (06 Marks)
- c. State and prove De Morgan's theorem using two variable. (08 Marks)

Module-4

- 7 a. Bring out differences between flip flops and latches.(04 Marks)b. Explain SR flipflop with circuit diagram and truth table.(06 Marks)
 - c. With a neat block diagram explain the architecture of 8051 microcontroller. (10 Marks)

OR

8 a. Explain the operation of NAND gate latch with circuit and truth table. (10 Marks)

b. What is stepper motor? With a neat block diagram, explain the working principle of microcontroller based stepper motor control system.

Module-5

		<u>Module-5</u>	
9 a	. De	efine communication. With neat:block diagram, explain the elements of commu	nication
		system. ;.	(06 Marks)
	b.	Derive an expression for amplitude modulation and draw the necessary waveforms.	
			(08 Marks)
	c.	What is transducer? Compare the active and passive transducers.	(06 Marks)
10	a. E	Bring out the difference between amplitude modulation and frequency modulation.	
		•	(06 Marks)
	b. I	If a FM wave represented by the equation $V = 10 \sin(8x \ 10^8 + 4 \sin 1000t)$, calculate	:
		i) Carrier frequency (ii). Modulating frequency	
1		iii) Modulation index Security iv) Band width	(06 Marks)
	C. V	With necessary diagram and equations, explain the following:	
		i) Piezo-electric transducer	
		ii) LVDT.	(08 Marks)