

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- III EXAMINATION – SUMMER 2020

Subject Code: 2130305

Date: 29/10/2020

Subject Name: ANALOG CIRCUITS-I

Time: 02:30 PM TO 05:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

| | | MARKS |
|------------|---|-----------|
| Q.1 | (a) Draw and explain negative and positive clipper. | 03 |
| | (b) List out the application for JFET. | 04 |
| | (c) Draw CE transistor configuration and give its input and output characteristics. Also derive the relation between current gain of CE, CB and CC configuration. | 07 |
| Q.2 | (a) Compare MOSFET with JFET. | 03 |
| | (b) Derive relationship between α_{dc} and β_{dc} of a transistor. | 04 |
| | (c) What is biasing? Why biasing is required for transistor? List biasing methods for transistor. Draw and explain the circuit of voltage divider biasing | 07 |
| | OR | |
| | (c) Draw and explain P-channel JFET. | 07 |
| Q.3 | (a) What do you mean by feedback? Explain why series voltage feedback connection is mostly used | 03 |
| | (b) Explain series voltage feedback in detail. | 04 |
| | (c) Draw and explain N-channel D – MOSFET. | 07 |
| | OR | |
| Q.3 | (a) Define 1) CMRR 2) Slew Rate 3) Input offset voltage | 03 |
| | (b) Draw the block diagram of an op-amp and write the function of each block in details. | 04 |
| | (c) Describe the log amplifier using op-amps. | 07 |
| Q.4 | (a) Why open loop configuration is not used for linear applications? | 03 |
| | (b) Write ideal and practical values of any four characteristics of an op – amp. | 04 |
| | (c) Draw the circuit of a V-I converter and derive an expression for the output current in terms of input voltage | 07 |
| | OR | |
| Q.4 | (a) Compare between Schmitt Trigger and Comparator. | 03 |
| | (b) Draw the circuit diagram of close loop non-inverting amplifier and derive expression of its voltage gain. | 04 |
| | (c) Draw the circuit diagram of basic integrator and practical integrator and derive expression. | 07 |
| Q.5 | (a) Draw the circuit diagram for basic triangular square wave generator. | 03 |
| | (b) Draw and explain Window detector using IC 741. | 04 |
| | (c) Draw and explain Inverting Schmitt Trigger using IC 741. | 07 |

OR

- Q.5**
- | | | |
|-----|--|-----------|
| (a) | What do you mean by oscillator and explain its needs? | 03 |
| (b) | Explain the wein bridge oscillator in detail. | 04 |
| (c) | Draw the circuit diagram of differential amplifier using three op-amp and write its output equation. | 07 |

www.FirstRanker.com