

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- VI EXAMINATION – SUMMER 2020

Subject Code: 2161709
Date: 29/10/2020
Subject Name: Programmable Logic Controller
Time: 10:30 AM TO 01:00 PM
Total Marks: 70
Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) List 3 companies which manufacture PLC	03
	(b) List out 4 sensors/devices which can be used as digital inputs.	04
	(c) Draw and explain block diagram of PLC	07
Q.2	(a) List out 3 parts of PLC scan cycle.	03
	(b) State the full form of ROM, PROM, EPROM and EEPROM	04
	(c) Write a PLC ladder program for level control of tank (i.e. empty and fill the tank) using latch/unlatch instruction and without using latch/unlatch instruction.	07
	OR	
	(c) Three conveyors fed a main conveyor. The count from each feeder conveyor is fed into an input register in PLC. Construct a PLC program to obtain the total count of parts on the main conveyor. Use a timer to update total count every 15 seconds.	07
Q.3	(a) Prepare a ladder logic for the following statement: Switch 8 and Switch 11, plus either switch 22 or switch 34, must be on for output 67 to be on.	03
	(b) Draw a neat circuit diagram of PLC input module	04
	(c) Explain in detail timing diagram and application of On delay timer	07
	OR	
Q.3	(a) Make a ladder diagram for the following sequence: When SW1 is closed, CR1 goes on. After CR1 goes on, SW2 can turn CR2 on. When CR2 goes on, PL1 goes off.	03
	(b) Draw a neat circuit diagram of PLC output module	04
	(c) Explain in detail timing diagram and application of Off delay timer	07
Q.4	(a) Explain how JUMP instructions differs from the SKIP and MCR Functions.	03
	(b) Explain up counter	04
	(c) Write a ladder program to turn light on only if a PLC counter has a value of 45 or 78.	07

OR

- Q.4** (a) Write a Ladder program to convert any binary number to BCD. **03**
(b) Explain down counter **04**
(c) Write a ladder program to transfer data in 7 registers starting from IR0100 to other 7 holding register starting from HR0200. **07**
- Q.5** (a) Prepare ladder logic to implement AND, OR and NOT logic gates **03**
(b) Describe various levels of industrial control **04**
(c) Explain in detail application of sequencer function to control Dishwasher **07**
- OR**
- Q.5** (a) List out 3 languages in which PLC can be programmed. **03**
(b) List 4 things which are done for preventive maintenance of PLC **04**
(c) Draw and explain the block diagram of PID module and explain various PID tuning methods. **07**
