

# GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- IV EXAMINATION – SUMMER 2020

**Subject Code: 2141706**

**Date: 29/10/2020**

**Subject Name: ANALOG SIGNAL PROCESSING**

**Time: 10:30 AM TO 01:00 PM**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
<b>Q.1</b>	(a) Draw only symbol and block diagram of op-amp.	<b>03</b>
	(b) Enlist Ideal characteristics of an Op-Amp.	<b>04</b>
	(c) Explain the following terms: (i) Input offset voltage (ii) Differential Input resistor (iii) CMRR (iv) SVRR (v) output voltage swing (vi) Large signal voltage gain (vii) Input bias current.	<b>07</b>
<b>Q.2</b>	(a) Explain Voltage to Current Converter with Floating Load.	<b>03</b>
	(b) Draw an op-amp based differential amplifier circuit and obtain expression for its differential gain.	<b>04</b>
	(c) Explain summing, scaling and averaging amplifier using Non-inverting configuration of operational amplifier.	<b>07</b>
	<b>OR</b>	
	(c) Derive the gain formula of Voltage shunt amplifier.	<b>07</b>
<b>Q.3</b>	(a) Explain Positive Clamper circuit.	<b>03</b>
	(b) Draw the circuit: 1. Wide band Pass filter and 2. Narrow band pass filters.	<b>04</b>
	(c) What is DAC? Draw and explain binary weighted resistor DAC.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Explain Positive clipper circuit.	<b>03</b>
	(b) Draw the circuit diagram: (1) All pass filter. (2) High pass filter.	<b>04</b>
	(c) Explain integrator circuit along with circuit diagram.	<b>07</b>
<b>Q.4</b>	(a) What is the offset-minimizing resistor ROM?	<b>03</b>
	(b) Explain the offset voltage compensating network for non-inverting amplifier.	<b>04</b>
	(c) Explain basic differentiator and practical differentiator circuit in detail.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) Draw oscillator block diagram and write principles.	<b>03</b>
	(b) Explain the Phase shift oscillator.	<b>04</b>
	(c) Explain Instrumentation amplifier using three op-amps for resistive transducer and bridge.	<b>07</b>
<b>Q.5</b>	(a) Explain Logarithmic amplifier.	<b>03</b>
	(b) Explain Wien bridge oscillator.	<b>04</b>
	(c) Draw and explain the 555 timer pin connection diagram and block diagram.	<b>07</b>
	<b>OR</b>	
<b>Q.5</b>	(a) Explain in brief: Schmitt trigger circuit.	<b>03</b>
	(b) Draw and explain the working of isolation amplifier.	<b>04</b>
	(c) Explain the working of 555 timers as an astable multivibrator with block diagram and waveforms.	<b>07</b>