

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER- IV EXAMINATION – SUMMER 2020****Subject Code: 2141706****Date: 29/10/2020****Subject Name: ANALOG SIGNAL PROCESSING****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Draw only symbol and block diagram of op-amp.	03
	(b) Enlist Ideal characteristics of an Op-Amp.	04
	(c) Explain the following terms: (i) Input offset voltage (ii) Differential Input resistor (iii) CMRR (iv) SVRR (v) output voltage swing (vi) Large signal voltage gain (vii) Input bias current.	07
Q.2	(a) Explain Voltage to Current Converter with Floating Load.	03
	(b) Draw an op-amp based differential amplifier circuit and obtain expression for its differential gain.	04
	(c) Explain summing, scaling and averaging amplifier using Non-inverting configuration of operational amplifier.	07
	<b>OR</b>	
	(c) Derive the gain formula of Voltage shunt amplifier.	07
Q.3	(a) Explain Positive Clamper circuit.	03
	(b) Draw the circuit: 1. Wide band Pass filter and 2. Narrow band pass filters.	04
	(c) What is DAC? Draw and explain binary weighted resistor DAC.	07
	<b>OR</b>	
Q.3	(a) Explain Positive clipper circuit.	03
	(b) Draw the circuit diagram: (1) All pass filter. (2) High pass filter.	04
	(c) Explain integrator circuit along with circuit diagram.	07
Q.4	(a) What is the offset-minimizing resistor ROM?	03
	(b) Explain the offset voltage compensating network for non-inverting amplifier.	04
	(c) Explain basic differentiator and practical differentiator circuit in detail.	07
	<b>OR</b>	
Q.4	(a) Draw oscillator block diagram and write principles.	03
	(b) Explain the Phase shift oscillator.	04
	(c) Explain Instrumentation amplifier using three op-amps for resistive transducer and bridge.	07
Q.5	(a) Explain Logarithmic amplifier.	03
	(b) Explain Wien bridge oscillator.	04
	(c) Draw and explain the 555 timer pin connection diagram and block diagram.	07
	<b>OR</b>	
Q.5	(a) Explain in brief: Schmitt trigger circuit.	03
	(b) Draw and explain the working of isolation amplifier.	04
	(c) Explain the working of 555 timers as an astable multivibrator with block diagram and waveforms.	07