

**GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER- IV EXAMINATION – SUMMER 2020**

**Subject Code: 3140915**

**Date: 04/11/2020**

**Subject Name: Power Electronics**

**Time: 10:30 AM TO 01:00 PM**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		Marks
<b>Q.1</b>	(a) Explain IGBT with its physical construction diagram and characteristics.	<b>03</b>
	(b) Draw the SCR static V-I characteristics and explain its behavior in forward conduction, forward blocking and reverse blocking modes.	<b>04</b>
	(c) Explain working of 1- $\phi$ semi converter with the help of voltage and current waveform under resistive load.	<b>07</b>
<b>Q.2</b>	(a) Compare the RC firing circuit and R firing circuit based on its circuit diagram.	<b>03</b>
	(b) Describe the effect of high switching frequency on harmonics spectrum in single phase full bridge inverter.	<b>04</b>
	(c) Derive the output voltage equation in case of buck and boost converter and draw the comparison.	<b>07</b>
	<b>OR</b>	
	(c) Draw the circuit diagram of three-phase full converter connected to RL load with continuous conduction. Draw the waveforms of output voltage, output current for firing angle equal to $60^\circ$ .	<b>07</b>
<b>Q.3</b>	(a) Write application of cycloconverters.	<b>03</b>
	(b) Write advantages and disadvantages of PWM technique to generate gate pulse.	<b>04</b>
	(c) Draw necessary waveforms and explain working of single phase full controlled rectifier circuit with R-L load.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Justify the statement why SCR is not suitable for dc to ac converter for low power applications.	<b>03</b>
	(b) Explain construction of Power MOSFET.	<b>04</b>
	(c) Describe the working of a single phase full bridge inverter with relevant circuit and waveforms for R-L Load.	<b>07</b>
<b>Q.4</b>	(a) Derive only expression of RMS output voltage of single phase full wave AC voltage controller with R load.	<b>03</b>
	(b) Write important features of sinusoidal pulse width modulation used in PWM inverters.	<b>04</b>

- (c) Explain working of 3 phase bridge inverter with star connected resistive load with  $180^\circ$  mode using gate signals, output phase voltage and line voltage. **07**

www.FirstRanker.com

www.FirstRanker.com

**OR**

- Q.4** (a) Describe the working of freewheeling diode in Phase controlled rectifier. **03**
- (b) Write a short note on matrix converter. **04**
- (c) Explain working of 3 phase bridge inverter with star connected resistive load with  $120^\circ$  mode using gate signals, output phase voltage and line voltage. **07**
- Q.5** (a) List the various voltage control techniques in DC-DC converters. **03**
- (b) Give four points of difference between on-off control and phase angle control. **04**
- (c) Explain the working principal of buck-boost converter with circuit diagram of different modes of operation. **07**

**OR**

- Q.5** (a) Draw the output voltage waveform of three-phase half-wave controlled rectifier with the R-load. **03**
- (b) State at least two reasons to control or eliminate the harmonics in inverters. List out different techniques to eliminate harmonics in inverter. **04**
- (c) Explain the parallel operation of SCR. **07**

www.FirstRanker.com