

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- IV EXAMINATION – SUMMER 2020

Subject Code: 3141706
Date: 26/10/2020
Subject Name: Analog Signal Processing
Time: 10:30 AM TO 01:00 PM
Total Marks: 70
Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

	MARKS
Q.1 (a) Define Following terms: <ol style="list-style-type: none"> 1. CMRR 2. SVRR 3. Slew Rate 	03
(b) Draw and explain in brief the internal block diagram of an Op-Amp.	04
(c) Derive the equation of voltage gain of differential amplifier using one Op-Amp (Closed loop configuration) with its circuit diagram.	07
Q.2 (a) Draw and explain Voltage follower circuit using an Op-Amp.	03
(b) Explain Bandwidth and Total output offset voltage for Inverting Amplifier with feedback.	04
(c) Derive the equation of voltage gain of Non-Inverting Summing amplifier using an Op-Amp with its circuit diagram.	07
OR	
(c) Draw and explain Voltage to Current converter with floating load using an Op-Amp.	07
Q.3 (a) Explain Subtractor circuit using an Op-amp.	03
(b) Explain Zero Crossing detector circuit using an Op-Amp with input/output waveforms.	04
(c) Explain Practical Differentiator circuit using an Op-Amp with its circuit diagram. Frequency response, input/output waveforms.	07
OR	
Q.3 (a) Draw and Explain Voltage limiter circuit using an Op-Amp.	03
(b) Draw and explain Sample and Hold circuit using an Op-Amp.	04
(c) Draw Op-amp based full wave rectifier (absolute value output) circuit. Explain its working with necessary input/output waveforms.	07
Q.4 (a) Design + 5V power supply using 7805 with its circuit diagram	03
(b) Explain adjustable voltage regulator using LM 317.	04

(c) Explain Instrumentation Amplifier using three Op-Amp Configuration and also derive the equation for the output voltage. 07

OR

- Q.4** (a) Explain Voltage controlled Oscillator (VCO) using IC 566. 03
- (b) Draw and explain Square wave generator circuit using an Op-Amp. 04
- (c) Explain Successive Approximation type Analog to Digital 07

- Q.5** (a) Explain All Pass filter. 03
- (b) Draw and explain Programmable Gain Amplifier. 04
- (c) Explain first order Low pass Butterworth Active filter with circuit diagram and derivation of its transfer function. 07

OR

- Q.5** (a) Explain Notch filter with its circuit diagram and necessary waveforms. 03
- (b) Explain Ramp Generator circuit using 555 timer in Astable mode operation. 04
- (c) Explain Monostable operation of 555 timer with its internal block diagram with its output voltage and capacitor voltage waveforms. 07
