

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-IV (NEW) EXAMINATION – WINTER 2020****Subject Code:2141002****Date:09/02/2021****Subject Name:Analog Circuit Design****Time:02:30 PM TO 04:30 PM****Total Marks:56****Instructions:**

1. Attempt any **FOUR** questions out of **EIGHT** questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

	MARKS
Q.1 (a) Enlist the ideal characteristics of OPAMP.	3
(b) List the parameter those affecting to the transistor at high frequencies.	4
(c) Draw the hybrid π model for CE configuration and explain it.	7
Q.2 (a) How op-amp is used as a summing amplifier?	3
(b) What is oscillator? What are the necessary conditions for the oscillations?	4
(c) Derive the expression for the frequency for the RC phase shift oscillator using transistor.	7
Q.3 (a) List the merits & Demerits of negative feedback.	3
(b) Define the following parameters of Op-Amp: (i) Slew rate (ii) CMRR (iii) Input offset voltage (iv) PSRR	4
(c) Derive the A_{vf} , R_{if} , & R_{of} for Voltage Amplifier.	7
Q.4 (a) Draw the block diagram of OPAMP.	3
(b) Draw the Block diagram of various Feedback topologies and explain the significance of each topology.	4
(c) For the voltage amplifier $A_v = 140$, $f_L = 200$ Hz, $f_H = 200$ KHz, $R_i = 2K\Omega$, $R_o = 4.7K\Omega$. When negative feedback is employed in it with $\beta = 0.4$, determine the A_{vf} , R_{if} , R_{of} , F_{LH} , F_{HF} .	7
Q.5 (a) What is precision rectifier?	3
(b) Explain the working of a Schmitt trigger using Op-amp.	4
(c) Explain the ideal integrator. What are the problems associated with this configuration? How it can overcome?	7
Q.6 (a) Explain operation of PLL with basic blocks.	3
(b) Explain instrumentation amplifier.	4
(c) Explain with the circuit diagram and waveforms, the monostable multivibrator using 555 timer.	7

- Q.7** (a) Classify filter on the basis their frequency response. **3**
(b) What is the difference between active and passive filters? **4**
(c) Show how Bi-quad circuit can be used as a universal filter? **7**
- Q.8** (a) Discuss magnitude and frequency scaling in filter design. **3**
(b) What do you mean by Voltage regulator? List different types of voltage regulators. **4**
(c) Design and explain the 2nd order low pass Butterworth filter. Derive the equation of gain for the same. **7**

www.FirstRanker.com