

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE- SEMESTER-VI (NEW) EXAMINATION – WINTER 2020****Subject Code:2160902****Date:27/01/2021****Subject Name:Power Electronics – II****Time:02:00 PM TO 04:00 PM****Total Marks: 56****Instructions:**

1. Attempt any FOUR questions out of EIGHT questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
<b>Q.1</b>	(a) Give classification of inverters. Draw circuit diagram of 1-phase half bridge center tapped inverter.	<b>03</b>
	(b) Draw phase voltage and line voltage waveform for 120° conduction of 3-phase H bridge inverter.	<b>04</b>
	(c) Draw circuit diagram of 3-phase cycloconverter. Comment on output harmonics in the cycloconverter.	<b>07</b>
<b>Q.2</b>	(a) Define modulation index. What is over modulation region?	<b>03</b>
	(b) Distinguish unipolar and bipolar PWM techniques.	<b>04</b>
	(c) Explain working of line commutated inverters. Give applications of line commutated inverters.	<b>07</b>
<b>Q.3</b>	(a) Give comparison of AC voltage controller with inverter.	<b>03</b>
	(b) Determine output harmonics for the ratio $f_c/f_m=15$ in sine PWM technique.	<b>04</b>
	(c) Explain effect of non-sinusoidal wave on the performance of rotating AC machine.	<b>07</b>
<b>Q.4</b>	(a) Compare space vector pulse width modulation (SVPWM) technique with sine PWM (SPWM) technique.	<b>03</b>
	(b) To eliminate 5 <sup>th</sup> harmonic using selected harmonic elimination technique, how many variables are to be determined?	<b>04</b>
	(c) Explain sine PWM technique with waveform. How output voltage varies with modulation index?	<b>07</b>
<b>Q.5</b>	(a) Distinguish load commutated cycloconverter with line commutated cycloconverter.	<b>03</b>
	(b) Give the reason to keep voltage to frequency ratio constant in induction motor drive. Suggest the converter that can be used for such applications.	<b>04</b>
	(c) Explain the basic principle of matrix converter. Compare it with inverter and cycloconverter.	<b>07</b>
<b>Q.6</b>	(a) Explain basic principle of cycloconverter.	<b>03</b>
	(b) Justify requirement of gating circuit. Mention its components.	<b>04</b>

- (c) Explain the working of single phase full wave ac voltage controller connected to R-L load. Derive its equation for the average output voltages. **07**

- Q.7** (a) Draw torque speed characteristics of induction motor. Define various region based on the slip value. **03**
- (b) Explain working principle of self-controlled synchronous motor drive using cycloconverter. **04**
- (c) Explain soft starting of induction motor. Which converter can be used for this purpose? **07**
- Q.8** (a) Explain rotor resistance control of induction motor. Suggest the converter that can be used for this application. **03**
- (b) Explain working principle of self-controlled synchronous motor drive using load commutated thyristor inverter. **04**
- (c) Explain static Kramer drive. **07**

\*\*\*\*\*

www.FirstRanker.com