

# GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-IV (NEW) EXAMINATION – WINTER 2020

**Subject Code:2140910**

**Date:11/02/2021**

**Subject Name:Digital Electronics**

**Time:02:30 PM TO 04:30 PM**

**Total Marks:56**

**Instructions:**

1. Attempt any FOUR questions out of EIGHT questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
<b>Q.1</b>	(a) Explain Octal to Binary encoder.	<b>03</b>
	(b) Explain Minterm and Maxterm.	<b>04</b>
	(c) State and prove De Morgan's theorems.	<b>07</b>
<b>Q.2</b>	(a) Define the following general characteristics of logic families. (i) Propagation delay time (ii) Fan-in (iii) Fan - out	<b>03</b>
	(b) Draw and explain with truth table Ex-OR and Ex-NOR gates.	<b>04</b>
	(c) Prove that NAND and NOR gates are universal gates.	<b>07</b>
<b>Q.3</b>	(a) Explain full- subtractor in brief.	<b>03</b>
	(b) Do as directed:-	<b>04</b>
	I. Add the following decimal numbers using 8421 BCD equivalent codes $679.6 + 536.8$	
	II. Multiply the binary numbers $(1011.01) \times (10.1)$	
	(c) Write a short note on XS-3 code.	<b>07</b>
<b>Q.4</b>	(a) Solve: (1) $(105.15)_{10} = (\text{_____})_2$ (2) $(378.93)_8 = (\text{_____})_2$ (3) $(B9F.AE)_{16} = (\text{_____})_8$	<b>03</b>
	(b) Explain Binary addition & subtraction with Example.	<b>04</b>
	(c) Explain Hamming codes. A seven bit Hamming code is received as 1110101. What is the correct code for even parity?	<b>07</b>
<b>Q.5</b>	(a) Differentiate between sequential circuit and combinational circuit.	<b>03</b>
	(b) Describe the operation of R-2R ladder D/A converter in brief	<b>04</b>
	(c) Minimize using K-map $f(A,B,C,D) = \Sigma(1,2,7,8,10,12,15) + d(0,5,6)$ also draw MSI circuit for the output.	<b>07</b>
<b>Q.6</b>	(a) What are Preset and Clear inputs with flipflop? Why are they provided with flipflop?	<b>03</b>
	(b) Explain operation of clocked S-R Flip-Flop.	<b>04</b>
	(c) Describe the working of look-ahead-carry adder.	<b>07</b>
<b>Q.7</b>	(a) Design a full adder circuit using decoder and multiplexer (4:1 MUX).	<b>03</b>
	(b) Compare between various types of ROM.	<b>04</b>
	(c) Explain working of Successive-Approximation-Register A/D converter. Compare it with Flash A/D converter.	<b>07</b>
<b>Q.8</b>	(a) State the applications of A to D converters	<b>03</b>
	(b) Explain concept of shift registers	<b>04</b>
	(c) Explain the concept of RAM. Explain working of any one type of RAM.	<b>07</b>

\*\*\*\*\*