

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(Electrical Engineering & Industrial Control) (2012 Onwards)
B.Tech.(EE/Electrical & Electronics/Electronics & Electrical) (2011 Onwards)
(Sem.-3)

CIRCUIT THEORY

Subject Code : BTEE-301

M.Code : 57092

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**1. Answer briefly :**

- a. Differentiate between independent and dependent sources.
- b. What do you mean by transient response? Explain.
- c. State reciprocity theorem.
- d. Find the Laplace transform of a unit ramp function.
- e. What is the significance of transfer function? Explain.
- f. Discuss the significance of circuit theory in engineering.
- g. Discuss the need of frequency domain analysis.
- h. What do you mean by network functions? Explain.
- i. Why network synthesis is required? Explain.
- j. List the advantages of m-derived filters.

SECTION-B

2. Determine the characteristic impedance and propagation constant of the symmetrical T-network.



- 3 Find the voltage across X and Y using Thevenin's theorem.

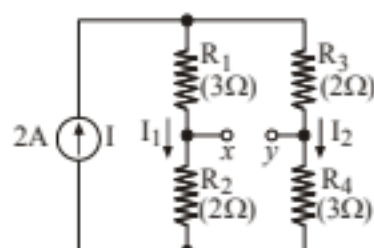


FIG.1

4. Discuss the importance of Laplace transform. Find the Laplace transform of $\cos \omega t u(t-t_0)$.
5. Discuss the significance of pole and zeros in a network. Also list the various restrictions on the pole and zero location in transfer functions.
6. What is the need of a filter? Discuss in detail high pass, low pass, band pass and band reject filters.

SECTION-C

7. Find the current in 10ohm resistor using superposition theorem.

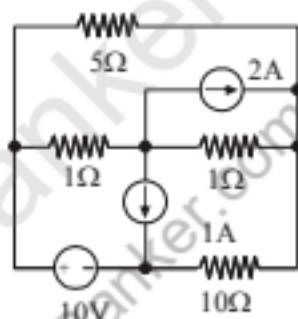


FIG.2

8. Find V_2/V_1 and V_2/I_1 of the figure shown below :

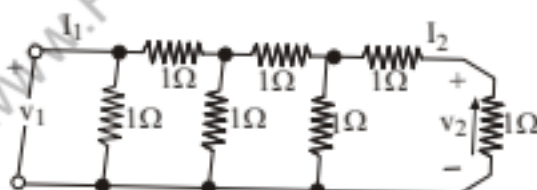


FIG.3

9. Explain the following :
- Design of constant K filter
 - Convolution theorem

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.