

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(EE)/(Electrical & Electronics)/(Electronics & Electrical) (2011 Onwards)

B.Tech.(Electrical Engineering & Industrial Control) (2012 Onwards)

(Sem.-3)

ELECTRONIC DEVICES AND CIRCUITS

Subject Code : BTEE-304

M.Code : 57095

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**1) Answer briefly :**

- a) State few applications of Zener diode.
- b) Find the base current for CE transistor circuit if $I_c = 80\text{mA}$ and $\beta = 170$.
- c) State Miller's theorem.
- d) Define conversion efficiency of power amplifier.
- e) State the Barkhausen criterion for an oscillator.
- f) Draw the structure of UJT.
- g) List the types of multivibrator.
- h) What is the need of summing amplifier?
- i) List out some advantages of double tuned amplifier.
- j) What is meant by saturation region?



SECTION-B

- 2) Derive the expression for the space charge or transition capacitance of PN diode with reverse bias with a neat diagram.
- 3) Explain Zener diode as a voltage regulator.
- 4) Explain how the amplification factor, input impedance, output impedance and bandwidth are modified with negative feedback.
- 5) What is MOSFET? Explain the construction and characteristics of N- channel MOSFET with the help of suitable diagram.
- 6) Explain the working of 555 timer as oscillator.

SECTION-C

- 7) Briefly explain voltage -series feedback amplifier with neat diagram and derive an expression for input output resistance.
- 8) Design a RC phase shift oscillator to generate 5kHz sine wave with 20V peak to peak amplitude. Assume $h_{fe} = \beta = 150$, $C = 1.5\text{nf}$, $h_{re} = 1.2\text{k}\Omega$.
- 9) Write the ac equivalent circuit for voltage divider JFET configuration and determine Z_i , Z_o and A_v .

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.