

[illegible]

SECTION-B

- 2) Derive the expression for the space charge or transition capacitance of PN diode with reverse bias with a neat diagram.
- 3) Explain Zener diode as a voltage regulator.
- 4) Explain how the amplification factor, input impedance, output impedance and bandwidth are modified with negative feedback.
- 5) What is MOSFET? Explain the construction and characteristics of N- channel MOSFET with the help of suitable diagram.
- 6) Explain the working of 555 timer as oscillator.

SECTION-C

- 7) Briefly explain voltage -series feedback amplifier with neat diagram and derive an expression for input output resistance.
- 8) Design a RC phase shift oscillator to generate 5kHz sine wave with 20V peak to peak amplitude. Assume $h_{fe} = \beta = 150$, $C = 1.5\text{nf}$, $h_{re} = 1.2\text{k}\Omega$.
- 9) Write the ac equivalent circuit for voltage divider JFET configuration and determine Z_i , Z_o and A_v .

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.