

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(Electronics Engg.) (2012 Onwards)**B.Tech.(ECE)/(Electronics & Computer Engg.)/(ETE) (2011 Onwards)**
(Sem.-3)**ANALOG DEVICES & CIRCUITS****Subject Code : BTEC-301****M.Code : 57583****Time : 3 Hrs.****Max. Marks : 60****INSTRUCTIONS TO CANDIDATES :**

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A**Q1. Write briefly :**

- a) Explain how Zener diode can be used as a voltage regulator.
- b) What is the principle behind the working of an oscillator?
- c) Explain the working of a transistor as a switch.
- d) What do you mean by dc load line?
- e) Give the V-I characteristics of PN diode.
- f) Calculate I_c and I_E for a transistor that has $\alpha_{dc} = 0.99$ and $I_B = 150\mu A$. Determine the value of β_{dc} for the transistor.
- g) Define Transconductance of MOSFET.
- h) What is pinch off voltage?
- i) State Barkhausen criteria for oscillators.
- j) What is diffusion capacitance?



SECTION-B

- Q2. Explain the effect of using negative feedback on various parameters of amplifiers.
- Q3. What are h-parameters? Explain how these are used for making equivalent transistor model.
- Q4. Discuss the factors involved in the selection of I_c , R_c and R_E for a single stage common emitter BJT amplifier circuit, using voltage divider bias.
- Q5. Explain in detail with diagrams, the difference between LED and Photo-diodes.
- Q6. Explain construction, operation and characteristics of JFETs.

SECTION-C

- Q7. Explain the construction and working of MOSFET.
- Q8. Explain the working of Colpitts oscillator. Derive the expression for its frequency.
- Q9. Describe in detail with diagram and characteristics:
- a) UJT
 - b) RC phase shift oscillator.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.