

[illegible]

**SECTION-B**

2. Explain interface between TTL to CMOS circuit.
3. Design a 4-bit BCD adder using full adder and explain its structure and compute the circuit to add 1001 and 0101. Write the sum and carry outputs of the given binary number.
4. Select a  $4096 \times 8$  bit ROM memory to store a program. The memory chip has two chip select inputs and operates from a 5V d.c. power supply. How many pins are needed for the integrated circuit package? Draw a neat block diagram and label all the input and the output terminals in the ROM.
5. Design a  $5 \times 32$  decoder using  $3 \times 8$  decoder and summarize how many decoders are required for designing the circuit.
6. Explain the organization of ROM with suitable diagrams.

**SECTION-C**

7. A 5-bit D/A converter produces  $V_{OUT} = 0.2V$  for, a digital input of 0001. Find the value of  $V_{out}$  for an input of 11111.
8. Write a program to implement a BCD to Excess-3 code conversion using a PLA.
9. Explain in detail about the working of bipolar SRAM cell and single transistor DRAM cell with neat sketches.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**