

Roll No.

Total No. of Pages : 03

Total No. of Questions : 09

B.Tech.(EIE) (2011 & Onwards) (Sem.-3)
NETWORK ANALYSIS AND SYNTHESIS
Subject Code : EE-201
M.Code : 57004

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**1. Answer briefly :**

- a. What do you mean by periodic voltage? Explain.
- b. What is loop current? Discuss.
- c. State Superposition theorem.
- d. What is steady state response? Discuss.
- e. Why network analysis is required? Explain.
- f. What do you mean by Admittance function? Explain.
- g. What do you mean by pass band and stop band? Explain.
- h. Discuss the significance of poles and zeros.
- i. List the limitations of constant-K filters.
- j. Explain briefly the purpose and the scope of network synthesis.

SECTION-B

2. Find R to have the maximum power transfer in the circuit. Also obtain the amount of maximum power.

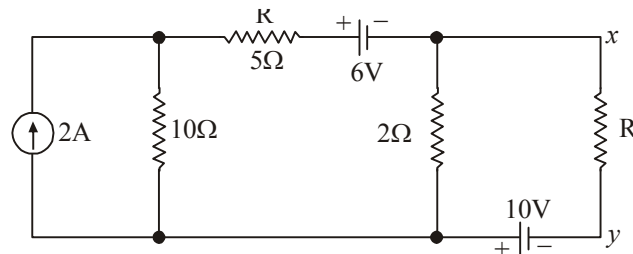


Fig.1

3. The T section constant $-K$ low pass filter has series inductance of 80 mH and shunt capacitance of $0.022\mu\text{F}$. Determine the cut-off frequency and nominal design impedance. Also design an equivalent π -section.
4. Find the expression for the voltage transfer ratio for the network shown below :

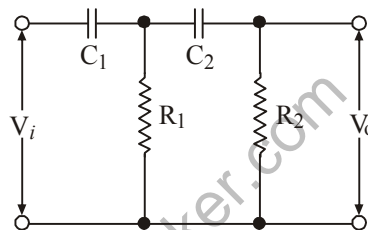


Fig.2

5. Find the current $i(t)$ in a series RC circuit having $R = 1 \text{ ohm}$, and $C = 0.5\text{F}$ when an exponential voltage $v = 10 e^{-t}$ is suddenly applied at $t = 0$.
6. If $u(t)$ is a unit step function, Find the Laplace transform of the following functions.
- $\sin \omega (t-t_0) u(t)$
 - $\sin \omega (t) u((t-t_0))$

SECTION-C

7. Explain the following :
- Design of m derived filters
 - Convolution theorem

8. Find the power loss in 1 ohm resistor using Thevenin's and verify the result Norton's theorem

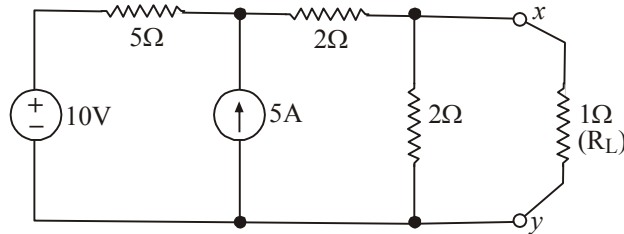


Fig.3

9. For the given function :

$$Z(s) = \frac{(s+1)(s+3)(s+5)}{s(s+2)(s+4)(s+6)}$$

Determine the Cauer, first and second forms of realisation.

www.FirstRanker.com

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.