

Roll No.

Total No. of Pages : 03

Total No. of Questions : 09

B.Tech.(ECE / Electronics & Computer Engg. / ETE) (2011 Onwards)

B.Tech. (Electronics Engg.) (2012 Onwards) (Sem.-3)

NETWORK ANALYSIS AND SYNTHESIS

Subject Code : BTEC-303

M.Code : 57585

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**Q1. Answer briefly :**

- a. State various properties of LC networks.
- b. Define h-parameters and draw its equivalent h-model.
- c. Find $f(\infty)$ if $F(s) = \frac{5s + 3}{s(s+1)}$
- d. A series RL circuit has $R = 10\text{K}\Omega$, $L = 10\text{mH}$ and $C = 1\mu\text{F}$. Find the Transfer function of the circuit.
- e. Check the positive realness of $F(s) = \frac{s^2 + 50s + 14}{s + 12}$
- f. Differentiate between Network Analysis and Network Synthesis. Name the methods to solve them.
- g. Using nodal analysis in Fig. 1 find the value of current in $20\ \Omega$ resistor.

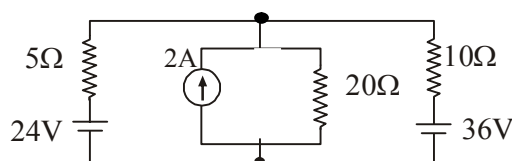


Fig.1

h. If two circuits X and Y are to be connected in cascade. Give the two port parameters of the combination with diagram cascade combination.

i. Find response of $H_{(s)} \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$ for step input.

j. Find condition for a 2-port network using Z and Y-Parameters to be reciprocal.

SECTION-B

Q.2 Find the value of Z_L in Fig. 2 so that maximum power is transferred to it. Also find the value of maximum power transferred.

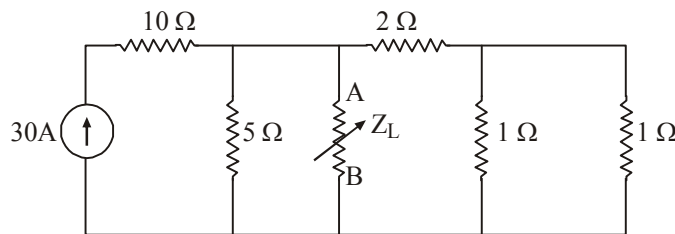


Fig. 2

Q.3 Find Y-parameters of the network of Fig. 3.

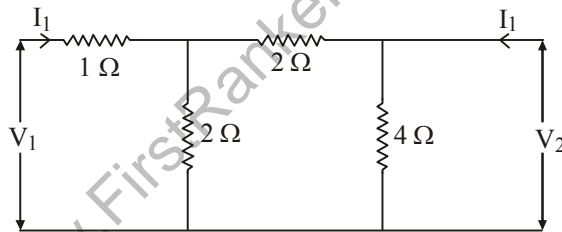


Fig. 3

Q.4 Steady state is achieved in the given circuit of Fig. 4 with switch, S open. Find the value of $I(t)$ for $t > 0$, if switch S is closed at $t = 0$.

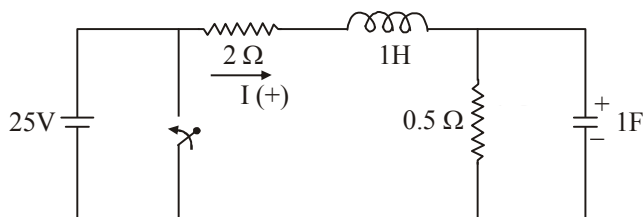


Fig. 4

Q.5 Using Nodal analysis, find I in the circuit of Fig. 5.

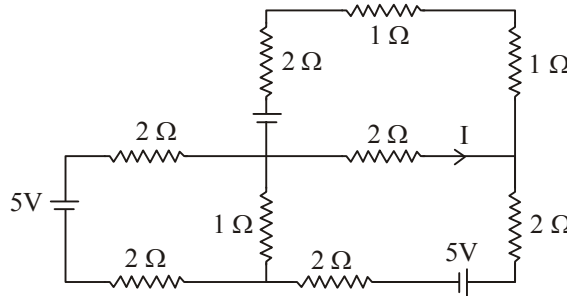


Fig. 5

Q.6 Classify filters and analyze any one type of filter in detail.

SECTION-C

Q.7 Synthesize a network using Foster-I and Foster -II forms for the impedance function :

$$Z(s) = \frac{s(s^2 + 9)}{(s^2 + 5)(s^2 + 13)}$$

Q.8 If an m-derived high pass filter has design impedance of 500Ω and cut off frequency of 3.5 KHz and infinite attenuation at 2.6 KHz, design the filter.

Q.9 Find current through Z_L in Fig. 6 using Norton's theorem and verify the result using Thevenin Theorem.

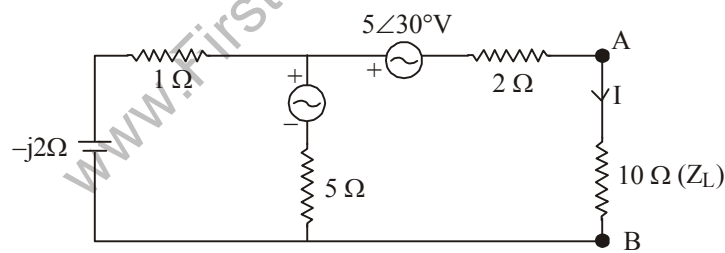


Fig. 6

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.