

Roll No. 

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 03

Total No. of Questions : 09

**B.Tech.(ECE / Electronics & Computer Engg. / ETE) (2011 Onwards)**
**B.Tech. (Electronics Engg.) (2012 Onwards) (Sem.-3)**
**NETWORK ANALYSIS AND SYNTHESIS**

Subject Code : BTEC-303

M.Code : 57585

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**SECTION-A**
**Q1. Answer briefly :**

- a. State various properties of LC networks.
- b. Define h-parameters and draw its equivalent h-model.
- c. Find  $f(\infty)$  if  $F(s) = \frac{5s+3}{s(s+1)}$
- d. A series RL circuit has  $R = 10K\Omega$ ,  $L = 10mH$  and  $C = 1\mu F$ . Find the Transfer function of the circuit.
- e. Check the positive realness of  $F(s) = \frac{s^2 + 50s + 14}{s + 12}$
- f. Differentiate between Network Analysis and Network Synthesis. Name the methods to solve them.
- g. Using nodal analysis in Fig. 1 find the value of current in  $20\Omega$  resistor.

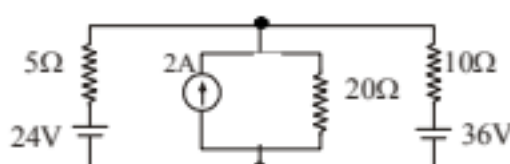


Fig.1

- h. If two circuits X and Y are to be connected in cascade. Give the two port parameters of the combination with diagram cascade combination.
- i. Find response of  $H(s) \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$  for step input.
- j. Find condition for a 2-port network using Z and Y-Parameters to be reciprocal.

### SECTION-B

- Q.2 Find the value of  $Z_L$  in Fig. 2 so that maximum power is transferred to it. Also find the value of maximum power transferred.

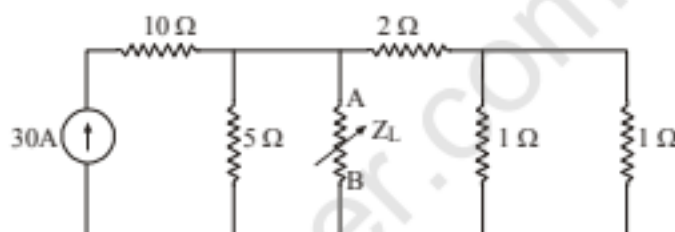


Fig. 2

- Q.3 Find Y-parameters of the network of Fig. 3.

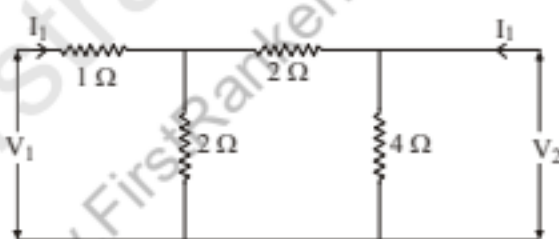


Fig. 3

- Q.4 Steady state is achieved in the given circuit of Fig. 4 with switch, S open. Find the value of  $I(t)$  for  $t > 0$ , if switch S is closed at  $t = 0$ .

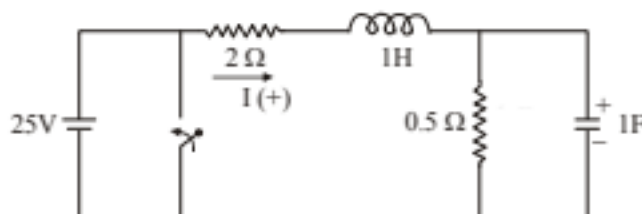


Fig. 4

Q.5 Using Nodal analysis, find  $I$  in the circuit of Fig. 5.

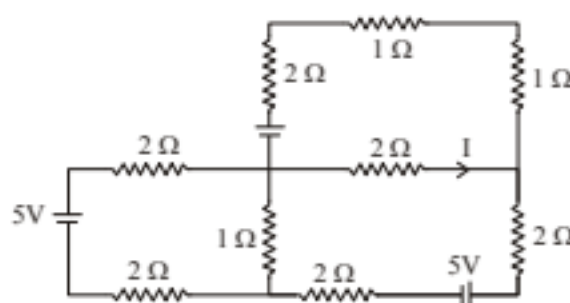


Fig. 5

Q.6 Classify filters and analyze any one type of filter in detail.

### SECTION-C

Q.7 Synthesize a network using Foster-I and Foster -II forms for the impedance function :

$$Z(s) = \frac{s(s^2 + 9)}{(s^2 + 5)(s^2 + 13)}$$

Q.8 If an m-derived high pass filter has design impedance of  $500\Omega$  and cut off frequency of 3.5 KHz and infinite attenuation at 2.6 KHz, design the filter.

Q.9 Find current through  $Z_L$  in Fig. 6 using Norton's theorem and verify the result using Thevenin Theorem.

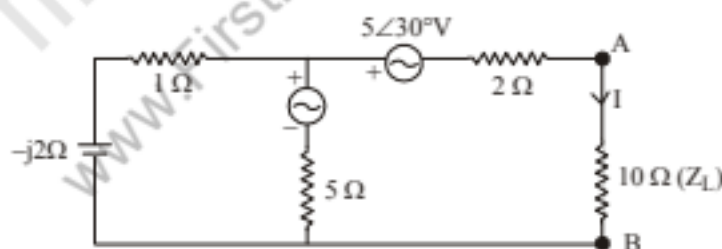


Fig. 6

**NOTE :** Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.