

Roll No. 

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

**B.Tech.(Automation & Robotics) (2011 & Onwards) (Sem.-3)****ELECTRONICS DEVICES AND DIGITAL CIRCUITS**

Subject Code : BTAR-302

M.Code : 63002

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTION TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**SECTION-A****1. Answer briefly :**

- a. Why is capacitive coupling used to connect a signal source to an amplifier?
- b. Determine the base current for the CE transistor circuit if  $I_C = 80\text{mA}$  and  $\beta = 170$ .
- c. Define the transconductance of MOSFET.
- d. Give the advantages of switching regulator.
- e. Define slew rate and its significance.
- f. Draw the circuit diagram of OP-AMP as an integrator.
- g. Write the frequency equation for an astable multivibrator.
- h. Define propagation delay time.
- i. What is the difference between combinational and sequential circuits?
- j. What is the difference between Latch and a flip-flop?



**SECTION-B**

- Q2. Explain the Operation of common drain MOSFET amplifier. Draw and explain its V-I characteristics.
- Q3. Explain the working of CE amplifier. Also draw its V-I characteristics.
- Q4. Draw the circuit diagram of Op-Amp as an inverting amplifier and derive the expression for output voltage.
- Q5. Minimize the function given below by means of Quine-McClusky method and realize it With NAND gates.

$$f = \sum (0,1,2,7,8,9,14) + \sum \phi (4,6,12,15)$$

- Q6. With suitable example, design a sequential circuit using JK-flip-flop.

**SECTION-C**

- Q7. (a) Design a 4-bit ripple counter using negative edge triggered JK flip-flop.
- (b) Explain the working principle of dual slope A/D converter.
- Q8. Describe the 555IC. Design an astable multivibrator circuit to generate output pulses 25%, 50% duty cycle using a 555 timer IC. With choice  $C = 0.01\mu\text{F}$  and frequency as 4.0 KHz.
- Q9. Write short notes on **any two** :
- (a) Switching regulators
- (b) Schmitt trigger
- (c) V-I converters

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**