

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(ECE / ETE) (2011 Onwards) (Sem.-4)

PULSE WAVE SHAPING AND SWITCHING

Subject Code : BTEC-405

M.Code : 57597

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES:

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.
4. Any missing data can be assumed appropriately.


SECTION-A**1. Answer briefly :**

- a) Differentiate between RC low pass and RC high pass filter.
- b) Write the output voltage expression and draw input and output waveform for the input voltage ($V_m \sin \omega t$) applied to a pure inductor.
- c) What is the role of feedback in electronics circuits.
- d) What do you mean by self bias bistable multivibrator?
- e) What is the difference between average and RMS values.
- f) Define resolution time in multivibrator.
- g) Define switching time in PN diode.
- h) Define UTP and LTP.
- i) Differentiate between linear and non-linear wave-shaping circuits.
- j) List the applications of attenuator.



SECTION-B

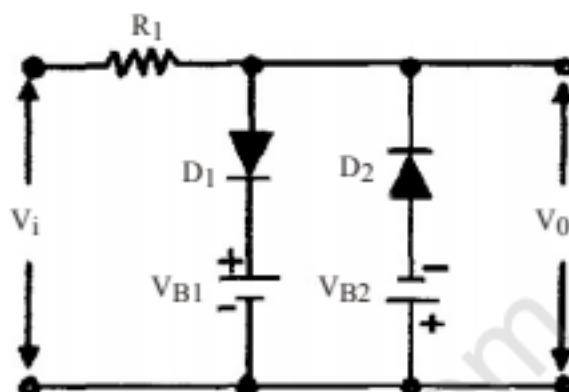- Q2. The fig shows double Clipper circuit. Determine its output waveform. Assume diode drop of 0.7 V with sinusoidal input with ± 20 V. Also V_{B1} and V_{B2} are 4V and 9V respectively.



- Q3. Explain the working of bistable multivibrator as "T" flip flop?
- Q4. State and prove Clamping Circuit Theorem.
- Q5. Explain the working of Schmitt trigger.
- Q6. How the BJT work as switch?

SECTION-C

- Q7. With waveforms, derive the expression for the frequency of oscillation of an astable multivibrator.
- Q8. Derive the response of low pass RC circuit for pulse input voltage and draw the waveform.
- Q9. Explain any two with necessary diagrams :
- Passive and active elements
 - Positive and negative clamper
 - Diode comparator

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.