

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

**B.Tech.(EE)/(Electrical & Electronics)/(Electronics & Electrical)
(2011 Onwards)****(Electrical Engineering & Industrial Control) (2012 Onwards)****(Sem.-5)****POWER ELECTRONICS****Subject Code : BTEE-504****M.Code : 70557****Time : 3 Hrs.****Max. Marks : 60****INSTRUCTION TO CANDIDATES :**

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A**1. Answer briefly :**

- a) Differentiate between holding and latching current in a Thyristor.
- b) What is the role of dv/dt in the operation of a Thyristor?
- c) Differentiate between Diac and Triac.
- d) What is the function of free wheeling diode?
- e) What is a LASCR?
- f) Write applications of a Thyristors.
- g) What is the importance of Surge current rating of a Thyristor?
- h) Draw turn on characteristics of a Thyristor.
- i) Draw snubber circuit.
- j) What is duty cycle of a chopper?

SECTION-B

- Q2 Explain two transistor model of a Thyristor.
- Q3 Compare power MOSFETs with BJTs.
- Q4 Discuss operation of single phase mid-point cycloconverter with R-L load for continuous conduction with relevant circuit diagram and necessary output waveforms.
- Q5 Describe the working of step down chopper and derive expression for output voltage.
- Q6 Draw and explain the simple SCR series inverter circuit employing class A type commutation with the help of important waveforms. State the limitations of this inverter.

SECTION-C

- Q7 What are the methods for voltage control within the inverters? Explain in detail with waveforms.
- Q8 a) Define string efficiency for series /parallel connected SCRs .Show the string efficiency of two series connected SCRs is less than one.
- b) Explain the difference between class A and class B commutation.
- Q9 A 230 V, 50 Hz, one pulse SCR controlled converter is triggered at a firing angle of 40° and the load current extinguishes at an angle of 210° . Find the current turn off time, average output voltage and average load current for
- a) $R = 5\Omega$ and $L = 2 \text{ mH}$.
- b) $R = 5 \Omega$, $L = 2 \text{ mH}$ and $E = 110 \text{ V}$.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.