

FACULTY OF SCIENCE**B.Sc. I – Semester (CBCS) Examination, November / December 2018****Subject : ELECTRONICS (Circuit Analysis)****Paper – I****Time : 3 hours****Max. Marks : 80****Part – A (5 X 4 = 20 Marks)**
(Short Answer Type)**Note : Answer any Five of the following questions.**

- 1 Define a phasor and explain the phasor representation of sinusoidal voltage.
- 2 Distinguish between active and passive networks.
- 3 State Millman's theorem.
- 4 Find the load resistance and current for maximum power transfer from a source of 100 volts dc having internal resistance of 50Ω .
- 5 Derive the expression for decay current in LR circuit and hence define time constant.
- 6 Mention the main characteristics of series resonance circuit at resonance.
- 7 Draw the circuit diagram of a low pass RC filter and draw its frequency response graph.
- 8 Explain the measurement of the phase angle using a CRO.

Part – B (4 X 15 = 60 Marks)
(Essay Answer Type)**Note : Answer all from the following questions.**

- 9 a) Define and derive the expression for the average and RMS value of a sinusoidal AC waveform.
OR
b) Explain the terms Node and Mesh. Explain mesh current and node voltage analysis to solve a two loop network with a single source in one branch.
- 10 a) State and prove Thevenin's theorem.
OR
b) State and prove reciprocity theorem.
- 11 a) Discuss the transient response of RC circuit with figures and derive the expression for the time constant.
OR
b) Explain the working of differentiator and integrator circuit with RC combination.
- 12 a) Draw the block diagram of a CRT and briefly explain its parts.
OR
b) What is resonance? Derive the expression for resonance frequency and quality factor of parallel resonant RLC circuit.