

120916474035

Code No. 3205

**FACULTY OF SCIENCE****B.Sc. V – Semester (CBCS) Examination, November / December 2018****Subject : ELECTRONICS (Digital Electronics)****Paper – V (DSC)****Time : 3 hours****Max. Marks : 60****Part – A (5 X 3 = 15 Marks)**  
(Short Answer Type)**Note : Answer any Five of the following questions.**

- 1 Convert decimal number 72905 to hexadecimal number.
- 2 Draw a circuit diagram of XOR gate and explain its working with truth table.
- 3 Show that  $(A + B)(\bar{A} + \bar{B}) = \bar{A}B + A\bar{B}$  using Boolean Algebra.
- 4 Explain sum of products (SOP).
- 5 Explain working of JK flip flop.
- 6 Explain Johnson Counter.
- 7 Explain 4-bit Asynchronous counter.
- 8 Distinguish between PROM and EPROM.

**Part – B (45 Marks)**  
(Essay Answer Type)**Note : Answer all from the following questions.**

- 9 a) Explain 1's compliment and 2's compliment method for subtraction. 11  
OR  
b) Draw the circuit diagram of parallel binary adder consisting of full adders and explain its operation.
- 10 a) State and explain the basic laws in Boolean algebra. 11  
OR  
b) Draw the circuit diagram of multiplexer and explain its operation.
- 11 a) Describe the working of Master Slave JK flip flop with neat circuit diagram. 11  
OR  
b) Discuss the various shift registers.
- 12 a) Describe the organization working of ROM. 12  
OR  
b) Explain working of decade counter with truth table and timing diagrams.

\*\*\*\*\*