

Roll No. 

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

Total No. of Pages : 02

Total No. of Questions : 07

**B.Sc.(IT) (2015 & Onward) (Sem.-2)**  
**DIGITAL CIRCUITS & LOGIC DESIGNS**

Subject Code : BSIT-204

M.Code : 72727

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and students have to attempt any FOUR questions.

**SECTION-A****1) Answer briefly :**

- a) When will be NAND gate output low? Write complete table.
- b) What is the Binary equivalent of the decimal number 368?
- c) What is the Decimal Equivalent of Hex number 1A53?
- d) Convert (9B2 - 1A) H to its decimal equivalent.
- e) What is difference between latch and flip-flop?
- f) What is a Multiplexer?
- g) Given the two binary numbers  $X=1010100$  and  $Y=1000011$ , perform the subtraction  $X-Y$ ,  $Y-X$  using 1's complement.
- h) State the commutative property of Boolean algebra.
- i) Prove that  $ABC + ABC' + AB'C + A'BC = AB + AC + BC$
- j) State the limitations of Karnaugh Map.



**SECTION-B**

2. What is a Logic gate? Give the classification of logic families. Which gates are called as the universal gates? What are its advantages?

3. a) Explain about Boolean expression. Simplify the Boolean expression

$$F = C(B + C)(A + B + C).$$

- b) Explain SOP and POS forms in detail.

4. What is K-map? Simplify the following expression into sum of products using Karnaugh map

$$F(A,B,C,D) = \Sigma (1,3,4,5, 6, 7, 9, 12, 13).$$

5. Explain Flip Flop. Show how a JK flip-flop can be constructed using a T flip-flop and other logic gates.
6. What is a Counter? What is the difference between Asynchronous counter and Synchronous counter?
7. What is the working of multiplexer and demultiplexer? What are their applications and advantages?

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**