

**B.C.A. (Part—I) Semester—II Examination**  
**2ST3 : DIGITAL TECHNIQUES—II**

Time : Three Hours]

[Maximum Marks : 60

- Note :—** (1) All questions are compulsory.  
(2) Draw neat diagrams wherever necessary.  
(3) Due credit will be given to neatness.

1. (A) What is D-Flip-Flop ? Explain with Diagram and Truth Table. 6  
(B) Explain construction and working of astable multivibrator with suitable diagram. 6

**OR**

2. (A) Define Flip-Flop and differentiate RS and CLKRS Flip-Flop. 6  
(B) Explain :  
(i) Monostable transistorized multivibrator  
(ii) Bistable transistorized multivibrator. 6

3. (A) What is Counter ? Explain Asynchronous 4-bit Counter with Diagram and Truth Table. 6  
(B) Explain up-down counters with suitable diagram. 6

**OR**

4. (A) State and explain applications of Modified Asynchronous Counter. 6  
(B) Draw and explain the diagram of IC 7493. 6  
5. (A) Explain :  
(i) SISO  
(ii) PISO. 6  
(B) Explain IC version of Shift register-7495 with connection diagram. 6

**OR**

6. (A) Explain the working of Ring Counter with neat diagram. 6  
(B) What is Johnson's Counter ? Explain with Connection Diagram and Truth Table. 6  
7. (A) Explain difference between Primary and Secondary Memory. 6  
(B) Explain :  
(i) RAM  
(ii) ROM  
(iii) EPROM. 6

**OR**

8. (A) Explain static RAM Cell with suitable diagram. 6  
(B) What is meant by Winchester disk ? Explain. 6  
9. (A) What is A/D and D/A converter ? Explain the working of weighted resistor type D/A Converter. 6  
(B) Draw and explain IC ADC 0808 with block diagram. 6

**OR**

10. (A) Draw and explain IC DAC 0808 with suitable diagram. 6  
(B) Draw the block diagram of successive approximation type A/D Converter and explain. 6

