

Code: 13A02803

B.Tech IV Year II Semester (R13) Regular Examinations April 2017

**HVDC TRANSMISSION**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

1 Answer the following: (10 X 02 = 20 Marks)

- What are the types of DC links?
- Draw the cost Vs distance curve of ac and dc transmission.
- What are the assumptions made to simplify the analysis of Graetz circuit?
- What is commutation voltage of valves?
- Explain overlap angle and extinction angle.
- What will be the current regulation in inverter side?
- Define total harmonic distortion.
- Write the characteristics of harmonics.
- What are the reasons for over voltages in HVDC systems?
- List out some methods, which can be used for over current protection.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- Compare AC & DC transmissions in detail.
  - Explain the major components of a HVDC transmission in converter station unit.

**OR**

- Explain in detail about the planning of HVDC transmission and explain the procedure for the selection of voltage level for a fixed power transfer.

**UNIT – II**

- Derive the expression for input power, output power and power factor of 12 pulse bridge converter with delay angle ( $\alpha$ ), assume there is no overlap.

**OR**

- Explain the choice of converter configuration for any pulse number.

**UNIT – III**

- Discuss in detail about the converter control characteristics of HVDC system.

**OR**

- Explain constant current, extinction angle and ignition angle control methods.

**UNIT – IV**

- Explain the need to employ filter circuit in HVDC systems. Derive an expression for minimum cost of tuned AC filter used in HVDC systems.

**OR**

- Write short notes on telephone influence factor and telephone harmonic form factor.
  - Discuss in detail the design of a high pass filter.

**UNIT – V**

- Explain the method of protection against over currents and mention the causes of over voltages in a converter station.

**OR**

- Explain short circuit in bridge rectifier with required short circuit current expressions and draw the voltage and current waveforms during short circuit.