

B.Tech IV Year II Semester (R15) Regular Examinations April 2019

**LOW POWER VLSI CIRCUITS & SYSTEMS**

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Define sub-threshold swing.
  - (b) Define channel length modulation.
  - (c) What is meant by fringing field capacitance?
  - (d) What are the disadvantages of resistive load inverter?
  - (e) What are the drawbacks of parallelism approach?
  - (f) What is the effect of feature scaling on power dissipation?
  - (g) List out the methods to minimize switched capacitance.
  - (h) What is meant by molecule in Transmeta Crusoe processor?
  - (i) Draw the AND gate using adiabatic logic.
  - (j) How multiple threshold voltages can be achieved in a circuit?

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) Explain the principles and challenges in low power design.  
(b) List different sources of dynamic and static power dissipation.

**OR**

- 3 Explain the structure and operation of NMOS transistor and derive expression for drain current.

**UNIT – II**

- 4 Explain the operation of depletion load nMOS inverter and draw the VTC.

**OR**

- 5 (a) Discuss in detail about the CMOS transmission gates.  
(b) Discuss delay parameters of MOS transistors.

**UNIT – III**

- 6 (a) Derive an expression for short circuit power dissipation of a CMOS inverter.  
(b) Explain in detail about switching power dissipation.

**OR**

- 7 Explain the optimization procedures for low power dissipation at algorithm and architecture level.

**UNIT – IV**

- 8 Explain any three techniques that are used to reduce power at the logic level.

**OR**

- 9 Using Shannon's expansion principle, explain the pre-computation of adder-comparator circuit.

**UNIT – V**

- 10 (a) Explain variable threshold CMOS inverter circuit with a neat sketch.  
(b) What are the advantages and disadvantages of MTCMOS circuits?

**OR**

- 11 Explain the techniques used to minimize the software contribution to power dissipation.

\*\*\*\*\*