

www.FirstRanker.com



B.Tech I Year (R13) Regular Examinations June/July 2014

NETWORK ANALYSIS

(Common to ECE & EIE)

Time: 3 hours

1

Max. Marks: 70

Part – A (Compulsory Question)

Answer the following: (10 X 02 = 20 Marks)

- (a) A network has 7 nodes and 5 independent loops. The number of branches in the network is______.
- (b) The nodal method of circuit analysis is based on _
- (c) For a series R-C circuit excited by a d-c voltage of 10 V, and with time-constant τ s the voltage across C at time t = τ is given by _____.
- (d) The Q factor for an inductor L in series with a resistance R is given by____
- (e) The Q factor of a parallel resonance circuit consisting of an inductance of value 1 mH, capacitance of value 10⁻⁵F and a resistance of 100 ohms is _____.
- (f) Power in 5 Ω resistors is 20 W. The resistance R is_
- (g) A 2-port network using z-parameter representation is said to be reciprocal if___
- (h) Two inductors of value L₁ and L₂ are coupled by a mutual inductance M. By inter connection of the two elements, one can obtain a maximum inductance of ______.
- (i) A n-section filter comprises a series arm inductance of 20 mH & two shunt capacitors each of 0.16 micro farad. Calculate the attenuation at 15 KHz.
- (j) A second order band pass filter has a value of 10 for the ratio of center frequency to bandwidth. The filter can be realized with _____.





- 2 (a) Explain the terms: (i) Incidence matrix. (ii) Basic cutset.
 - (b) Obtain the Norton's equivalent at the terminals 1, 1' of the network shown in figure given below.



- 3 (a) Explain the terms: (i) Basic tie set. (ii) Node & mesh.
 - (b) State and explain the reciprocity theorem and verify the network shown in figure given below is reciprocal or not.



www.**FigstRan**ker.com

www.FirstRanker.com

- (a) Obtain the expression for frequency at which the voltage across the inductance becomes a maximum in a series RLC circuit. Explain what is meant by voltage magnification factor.
 - (b) Find the maximum power that can be transferred to the load resistance R_{L} in the circuit shown in figure given below.



- 5 (a) Find the expression for current of a series R-L-C circuit fed by constant DC voltage of 20 V with R = 4 Ω , L = 1 H and C = $\frac{1}{4}$ F. Assume initial conditions to be zero.
 - (b) Obtain the total current, branch currents and the power consumed by each branch. Draw the phasor diagram for the network shown in figure given below.



- 6 (a) Define resonance, anti resonance, quality factor. Deduce the resonant frequency of parallel RLC circuit.
 - (b) Compare series resonance and parallel resonance circuits. An RLC circuit consists of R = 1 k Ω , L = 100 mH, C = 10 μ F. If a voltage of 100 V is applied across the combination, determine resonant frequency, Q factor and bandwidth.
- 7 (a) Deuce the relation between bandwidth and resonant frequency.

anker.com

Code: 13A04101

4

(b) An inductance of 0.5 H a resistance of 5 Ω and a capacitance of 8 μ *F* are in series across a 220 V AC supply. Calculate the frequency at which the circuit resonates. Find the current at resonance bandwidth, half power frequencies and the voltage across capacitance of resonance.

8 (a) Obtain the hybrid parameters of the following 2-port network figure given below.



- (b) Derive the relation between Y and h parameters.
- 9 (a) Design a high pass filter with a cut-off frequency of 1 KHz with a terminated design impedance of 800 Ω .
 - (b) Obtain the transmission parameters for the following circuit figure given below. Verify your result for reciprocity condition. 5 j6 5



- 10 (a) What is the different between constant –k and m-derived filters?
 - (b) Design an m-derived π section high pass filter with a cut-off frequency of 10 KHz, R_k = 600 Ω and infinite attenuation frequency of 8 KHz.

OR

- 11 (a) Explain what is meant by constant k-filters. Classify them.
 - (b) Design an m-derived T section low pass filter having a design impedance of 600 Ω, cut-off frequency of 2,400 Hz and infinite attenuation at 2,500 Hz.

www.FirstRanker.com