

www.FirstRanker.com

www.FirstRanker.

B.Tech I Year (R13) Supplementary Examinations December 2019

ELECTRICAL CIRCUITS

(Electrical & Electronics Engineering)

Max. Marks: 70

Time: 3 hours

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
 - (a) Define about Active and Passive elements with examples
 - (b) When two branches having $(2+j10)\Omega$ and $(5+j20)\Omega$ are connected in parallel and their equivalent is in series with $(8+j30)\Omega$. Find the total equivalent impedance.
 - (c) Describe the importance of power factor.
 - (d) For half wave rectified alternating current, find form factor.
 - (e) Define and describe briefly about band width.
 - (f) Discuss briefly about Super Node with neat sketch.
 - (g) Write the statement of compensation theorem.
 - (h) Write any two applications of superposition theorem.
 - (i) List any two applications of Laplace transforms.
 - (j) Describe briefly about Line Spectra.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) Explain in detail about resistance, inductance and capacitance parameters.
 - (b) An iron ring 10 cm diameter and 15 cm² in cross section is wound with 250 turns of wire of flux density of 1.5 Web/m² and permeability 500. Find the exciting current, the inductance and stored energy. Find corresponding quantities when there is a 2 mm air gap.

OR

- 3 (a) Derive the relation between self and mutual inductances. Also, derive the expression for coefficient of coupling between two mutually coupled coils.
 - (b) Find the power dissipated at 6Ω resistor in the network shown below.



- 4 (a) Explain about how to calculate voltage and power in a balanced three phase circuit.
 - (b) For a half wave rectified alternating current find Average value, RMS value, Form factor and Peak factor. Find the average and RMS values when I_m is 3A.

OR

- 5 (a) Discuss in detail about unbalanced three phase delta circuits with inductive loads.
 - (b) Explain about two wattmeter method for measuring three phase power.

Contd. in page 2



www.FirstRanker.com

Code: 13A02101

UNIT – III

- 6 (a) Draw and explain in detail about the locus diagram for R-L-C series circuit.
 - (b) Write short notes on Graph, Tree and Link with examples.

OR

7 (a) In the circuit shown below, determine the power delivered to 4Ω resistor by mesh analysis.



(b) The reduced incidence matrix of a graph is given below. Draw the graph corresponding to it.

$$\begin{bmatrix} -1 & +1 & 0 & 0 & 0 & -1 \\ 0 & 1 & -1 & +1 & 0 & 0 \\ 0 & 0 & +1 & 0 & -1 & +1 \end{bmatrix}$$

UNIT – IV

8 (a) Find the z-parameters of the network shown below.



(b) State and explain in detail about the maximum power transfer theorem with an example.

OR

- 9 (a) Discuss in detail about transmission and hybrid parameters and also derive their relation for two port network.
 - (b) Verify reciprocity theorem with a suitable example.

UNIT – V

- 10 (a) Explain in detail about DC transient R-C series circuit.
 - (b) Describe in detail about trigonometric form and exponential form of Fourier series.

OR

- 11 (a) Discuss response of R-C networks for pulse excitation.
 - (b) Explain in detail about the transient response of R-L circuit for sinusoidal excitation.
