

www.FirstRanker.com

www.FirstRanker. Raf 3

## B.Tech I Year (R13) Supplementary Examinations December 2019

## NETWORK ANALYSIS

(Common to ECE & EIE)

Max. Marks: 70

Time: 3 hours

PART – A (Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
  - (a) Write the tie-set matrix of the circuit shown in figure below.



(b) Draw the Thevenin equivalent resistance for the given network.



- (c) A resistor in parallel with a capacitor absorbs 20 W when the combination is connected to a 240 V, 50 Hz source. If the power factor is 0.7 leading, what are the resistance and capacitance?
- (d) If a coil draws 0.5A from a 120 V, 60 Hz source at 0.7 lagging power factor, what are the coil resistance and inductance?
- (e) Determine the quality factor of a RLC series circuit  $R = 10\Omega$ ,  $C = 100\mu$ F and L = 0.01mH.
- (f) What values of inductor is to be used in a tank circuit to get a resonant frequency of 10 kHz and bandwidth of 1 kHz? The winding resistance is 30Ω.
- (g) Define the Z parameters.
- (h) Define ideal filter.
- (i) Give the relation between Decibel and Nepers.
- (j) Design a constant- K low pass filter (T-section and  $\pi$  section) having a cut-off frequency of 2 kHz to operate with a terminated load resistance of 500 $\Omega$ .

Contd. in page 2



www.FirstRanker.com

www.FirstRanker.Raf 3

PART - B(Answer all five units, 5 X 10 = 50 Marks)
(UNIT - I)

2 (a) Obtain the current  $I_x$  by Thevenin's theorem .



(b) Calculate the current through R<sub>1</sub> of the network using superposition theorem.



3 (a) A resistive network shown in figure, setup corresponding tie-set matrix and obtain KVL equation.



(b) A voltage source delivers 4A when the load connected is  $5\Omega$  and 2A when the load is  $20\Omega$ . What is the maximum power it can deliver, power transfer efficiency when it delivers 50 W?



4 (a) Calculate the currents  $i_1(t)$  and  $i_2(t)$  of the circuit shown. Assume initially relaxed condition and the switch is closed at t = 0.



(b) Three coils are connected in series. Derive the expression for the equivalent inductance.

OR

5 In the circuit shown, the initial value of the charge on the capacitor is 20 V. Calculate: (i) i(t) for t>0. (ii) Time constant.



Contd. in page 3

FirstRanker.com

Code: 13A04101

www.FirstRanker.com



## UNIT – III

- 6 (a) A coil of 10H and resistance of  $10\Omega$  is in with 100pF capacitor. The combination is connected across a generator of 100 V, having internal resistance of  $100 k\Omega$ . Determine: (i) Voltage across parallel circuit at resonance. (ii) Bandwidth.
  - (b) Derive the expression for resonant frequency for a tank circuit.

#### OR

- 7 (a) In a series resonant circuit the resistance is 6Ω, the resonant frequency is 4.1 x 10<sup>6</sup> rad/sec and the bandwidth is 10<sup>5</sup> rad/sec. Compute L and C of the network, half power frequencies and Q of the circuit.
  - (b) Distinguish between reactance, impedance, admittance and suceptance.

### UNIT – IV

8 (a) For the bridged T network shown, find the driving point admittance  $y_{11}$  and transfer admittance  $y_{21}$  with a 2 $\Omega$  load resistor connected across port 2.



(b) For the hybrid equivalent circuit shown, determine the current gain and voltage gain.



9

Find the z parameters for the circuit shown in figure below.



- 10 (a) Design a m-derived low pass filter having cut-off frequency of 2 kHz, design impedance of  $500\Omega$  and the resonant frequency 2100 Hz.
  - (b) Design a constant-k high pass filter having a cut-off frequency of 1 kHz with a load resistance of  $700\Omega$ .

OR

11 Design a m-derived high pass filter with a cut-off frequency 5 kHz ,design impedance  $500\Omega$  and  $\frac{m = 0.4}{m}$ 

# www.FirstRanker.com