

Code: 13A99101

B.Tech I Year (R13) Supplementary Examinations December 2017

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Common to CSE and IT)


Time: 3 hours

Max. Marks: 70

 Answer all the questions
 (Use single answer booklet only)


PART - A
UNIT - I

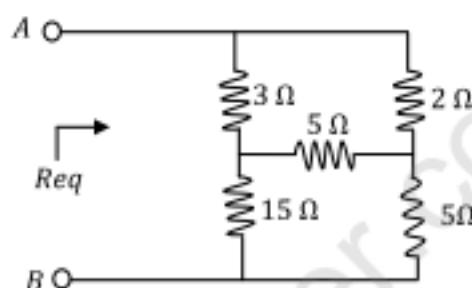- 1 Find the equivalent resistance between the terminals AB using Delta-Star transformation for the circuit shown below:




OR

- 2 Determine root mean square value, average value, peak factor and form factor for the following waveform.

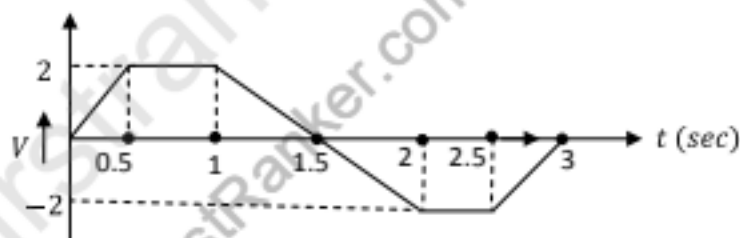
UNIT - II

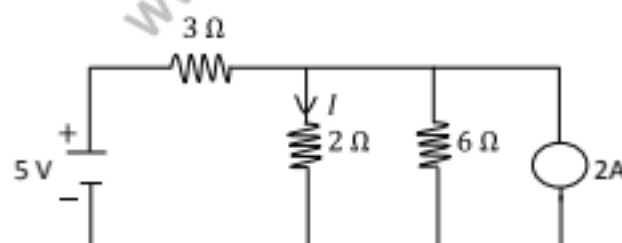- 3 Find the current I through 2Ω resistance using superposition theorem for the circuit shown below:



OR

- 4 A two part network has the following z - parameters. Find the h - parameters and transmission parameters: $Z_{11} = 1\Omega$; $Z_{12} = Z_{21} = -0.2\Omega$; $Z_{22} = 0.6\Omega$.

UNIT - III

- 5 Explain in detail the principle of operation and characteristics of DC motors.

OR

- 6 With a neat diagram, explain the construction of 3 - phase induction motor.

Contd. in page 2

**PART – B****UNIT – I**

- 7 Explain the operation of forward bias and reverse bias PN junction Diode.

OR

- 8 Explain the operation of π section filter with bridge rectifier and also derive an expression for its stability factor.

UNIT – II

- 9 Draw and explain the input and output characteristics of a transistor in CC configuration.

OR

- 10 Describe the kind of operation that takes place in the enhancement mode MOSFET. How does this differ from depletion mode type?

UNIT – III

- 11 Explain the working of Colpitts oscillator and derive an expression for frequency of oscillation for Colpitts oscillator.

OR

- 12 Give the characteristics of an ideal Op-Amp.
