

B.Tech I Year II Semester (R15) Regular & Supplementary Examinations May/June 2019

**ELECTRICAL CIRCUITS – I**

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*


- 1 Answer the following: (10 X 02 = 20 Marks)
  - (a) An incandescent lamp is rated for 110 V, 100 W. Using a suitable resistor how you can operate this lamp on 220 V mains.
  - (b) Define self-inductance and mutual inductance of a coil.
  - (c) Define form factor and peak factor.
  - (d) A voltage of 100 V is applied to a capacitor of 12  $\mu\text{F}$ . The current is 0.5 A. What must be the frequency of supply?
  - (e) What is the resonant frequency and bandwidth of a series RLC circuit whose  $R = 5\Omega$ ,  $L = 40\text{mH}$  and  $C = 1 \mu\text{F}$ .
  - (f) In a series RLC circuit, if the value of  $L$  and  $C$  are 10 mH and 0.1  $\mu\text{F}$ , determine the value of  $R$  to give critical damping.
  - (g) A load is connected to a network of the terminals to which load is connected,  $R_{th} = 10\Omega$  and  $V_{th} = 40 \text{ V}$ . Calculate the maximum power supplied to the load.
  - (h) List the applications of Norton's theorem.
  - (i) A two port network is characterized by  $V_1 = 8I_1 + 6I_2$  and  $V_2 = 10I_1 + 6I_2$ . Find the transmission parameters  $A$  and  $C$ .
  - (j) When a two port network is said to be reciprocal?

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

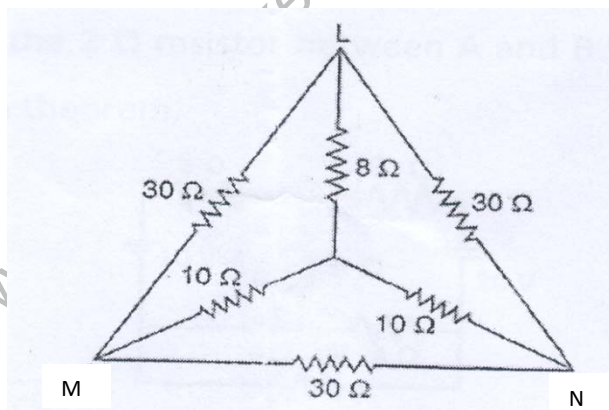
**UNIT – I**

- 2 For the network shown in figure below, find the equivalent resistance between the terminals M and N.



OR

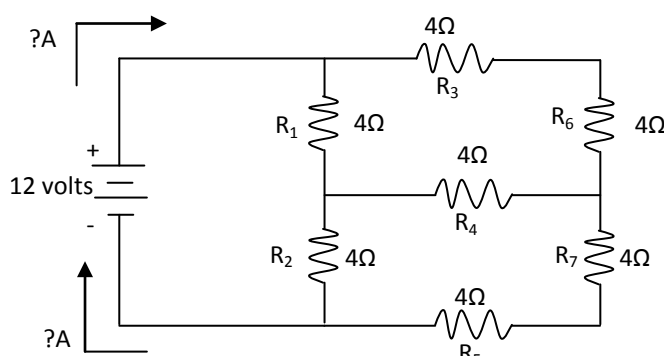- 3 For the circuit shown below, determine the current supplied by the 12 V d.c source.



Contd. in page 2

**UNIT – II**

- 4 A  $20\Omega$  resistor and a  $30\text{mH}$  inductor are connected in series across a  $300\text{ V}$ ,  $50\text{ Hz}$  a.c supply. Find: (i) Impedance of the circuit. (ii) Voltage across the resistor. (iii) Voltage across the inductor. (iv) Apparent power. (v) Active power. (vi) Reactive power.

**OR**

- 5 Two impedances  $(15-j10)\Omega$  and  $(10+j15)\Omega$  are connected in parallel. The supply voltage is  $200\text{ V}$ ,  $50\text{ Hz}$ . Calculate: (i) Admittance. (ii) Conductance. (iii) Susceptance. (iv) Total current. (v) Total power.

**UNIT – III**


- 6 A coil of resistance  $40\Omega$  and inductance  $0.75\text{H}$  forms part of a series circuit for which the resonant frequency is  $55\text{ c/s}$ . If the supply is  $250\text{ V}$ ,  $50\text{ c/s}$ . Find: (i) Line current. (ii) Power factor. (iii) Voltage across the coil.

**OR**

- 7 Derive the expression for resonant frequency and bandwidth for a series RLC resonant circuit.

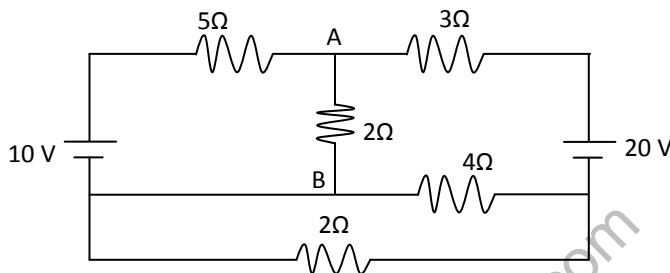
**UNIT – IV**

- 8 Find the current in the  $2\Omega$  resistor between A and B for the network shown below using Super Position theorem.



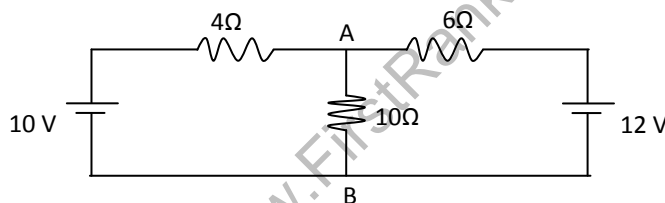
**OR**

- 9 Determine the current flowing through the  $10\Omega$  resistor by using Thevenin's theorem.



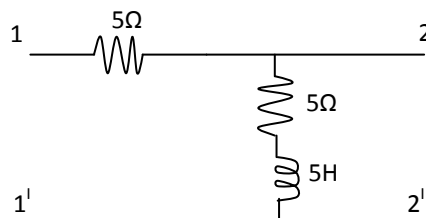**UNIT – V**

- 10 Obtain the admittance parameters of the network shown in figure below.



**OR**

- 11 Find the h-parameter for the network shown below.

