

B.Tech I Year II Semester (R15) Regular & Supplementary Examinations May/June 2019

NETWORK ANALYSIS

(Common to ECE & EIE)


Time: 3 hours

Max. Marks: 70


PART – A
(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

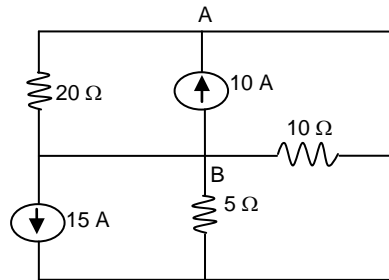(a) Determine the voltage drop across the 10Ω resistance in the circuit shown in figure.



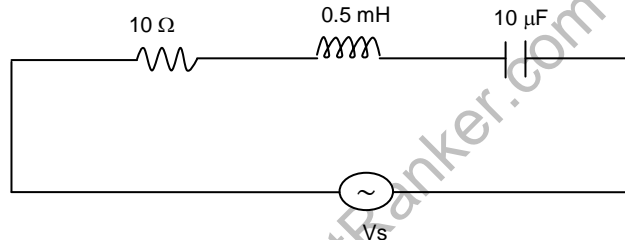- (b) State maximum power transfer theorem.
- (c) Distinguish between natural and forced response.
- (d) Write the differences between RL and RC transient circuits.
- (e) If the phase angle θ is 45° , what is the power factor?
- (f) Define instantaneous power and average power.
- (g) Determine the resonant frequency for the circuit shown in figure below.




- (h) Illustrate the concept of mutual inductance.
- (i) For a given $Z_{11}=3\Omega$, $Z_{12}=1\Omega$, $Z_{21}=2\Omega$ and $Z_{22}=1\Omega$, find the admittance matrix and the product of Δ_y and Δ_z .
- (j) For a two port network, define and relate Decibel and Neper.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

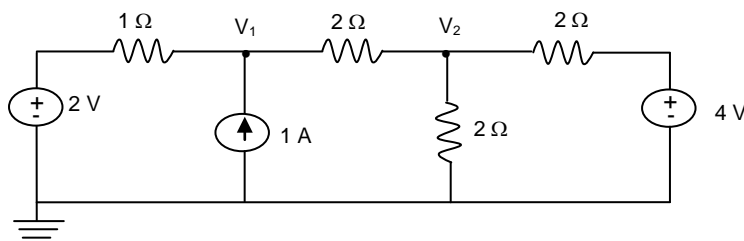
2 By applying the superposition theorem determine the node voltage V_1 and V_2 for the network shown in figure.



OR


Contd. in page 2

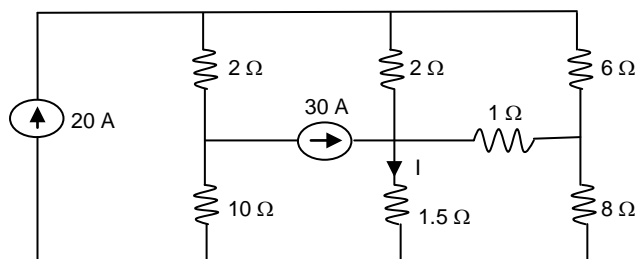- 3 Determine the current flowing through 1.5Ω resistor in the circuit shown in figure by loop analysis.




UNIT – II

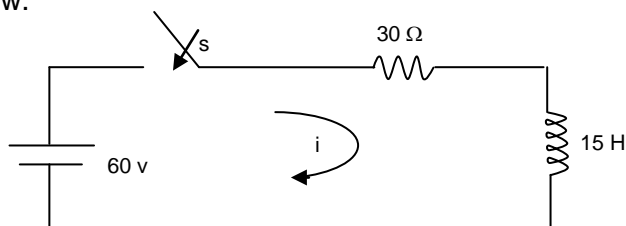- 4 (a) A series RL circuit with $R = 30 \Omega$ and $L = 15 \text{ H}$ has a constant voltage $V = 60 \text{ V}$ applied at $t = 0$ as shown in figure below.




Determine the current I , voltage across the resistor and inductor.

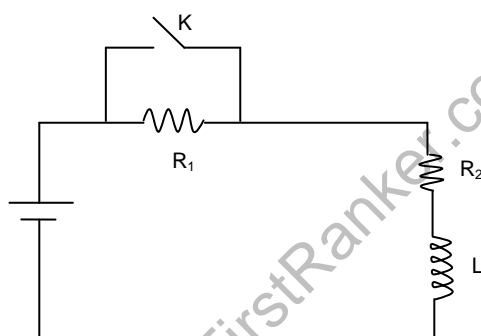- (b) In the given circuit shown in figure below, the switch k is closed at time $t = 0$, the steady state condition having reached preciously. Obtain the expression for the current in the circuit at any time t . If $R_1 = R_2 = 100 \Omega$, $v = 10 \text{ v}$ and $L = 1 \text{ H}$, calculate at time $t = 5 \text{ ms}$ (i) Current I . (ii) Voltage drop across R_2 . (iii) Voltage across L .



OR

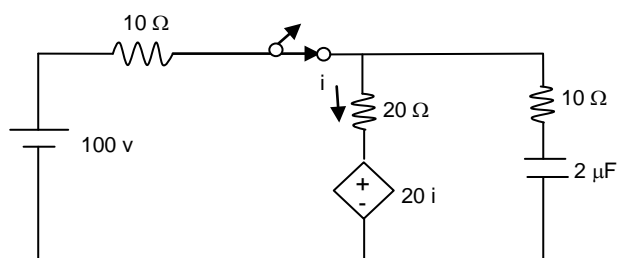- 5 (a) An RL series circuit is excited by a sinusoidal source $e(t) = 10 \sin 100t$ volts, by closing the switch at $t = 0$. Take $R = 10 \Omega$ and $L = 0.1 \text{ H}$. Determine the current $i(t)$ flowing through the RL circuit.
- (b) For the circuit shown in figure below, find the current equation when the switch is opened at $t = 0$.



Contd. in page 3


Code: 15A04201

R15
UNIT – III

- 6 With necessary derivations, illustrate the concept of instantaneous power, average power, apparent power and reactive power.

OR

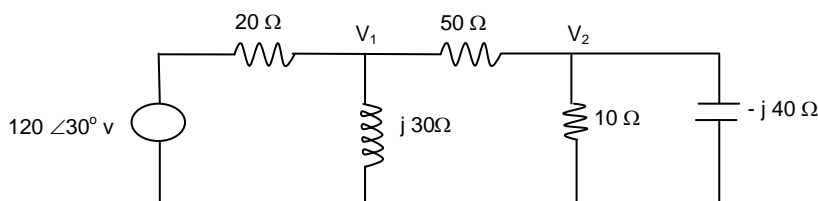
- 7 (a) For the circuit shown in figure below, find:
 (i) Real power dissipated by each element.
 (ii) The total apparent power supplied by the circuit.
 (iii) The power factor of the circuit



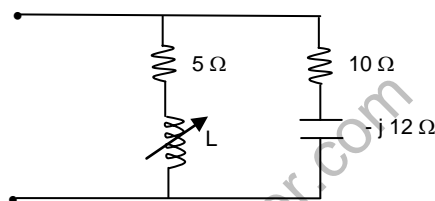
- (b) Two impedances $Z_1 = 10 \angle -60^\circ \Omega$ and $Z_2 = 10 \angle -70^\circ \Omega$ are in series and pass an effective current of 5A. Determine the active power, reactive power, apparent power and power factor.

UNIT – IV

- 8 (a) Find the value of L at which the circuit resonates at a frequency of 1000 rad/sec in the circuit shown in figure below.



- (b) A 50 Ω resistor is connected in series with an inductor having internal resistance, a capacitor and 100 V variable frequency supply as shown in figure below. At a frequency of 200 Hz, a maximum current of 0.7A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants.

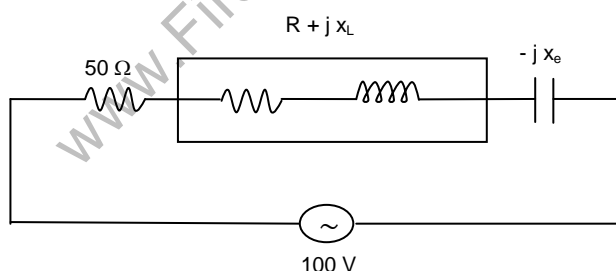
OR

- 9 (a) Derive the relation between bandwidth and quality factor.
 (b) Analyze ideal transformer circuits.

UNIT – V

- 10 Derive the Z-parameters of two port network. Relate Y, h and ABCD parameters with Z-parameter.

OR

- 11 (a) Derive the characteristic impedance of T-network.
 (b) Design a low pass filter (both π and T sections) having cut off frequency of 2 kHz to operate with a load resistance of 500 Ω.
