

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 03

Total No. of Questions : 18

B.Tech. (EE) (2018 Batch) (Sem.-3)

ELECTRICAL CIRCUIT ANALYSIS

Subject Code : BTEE-301-18

M.Code : 76381

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**Answer briefly :**

Q1 What are duality Networks?

Q2 Express Z-parameters in terms of Y-parameters.

Q3 State and derive maximum power transfer theorem.

Q4 Two parallel branches Z_1 and Z_2 take the current I_1 and I_2 as follows : $I_1 = 3.15 \angle 68^\circ \text{A}$; $I_2 = 12 \angle -45^\circ \text{A}$, find the complex power drawn from 17V supply.

Q5 Explain the importance of pole and zeroes in a transfer function.

Q6 Define : series and parallel resonances.

Q7 Find total inductance of three inductances in additive series combination with $L_1 = 2\text{H}$, $L_2 = 3\text{H}$ and $L_3 = 5\text{H}$, the mutual inductances are $M_{12} = 1\text{H}$, $M_{13} = 2\text{H}$ and $M_{23} = 0.5\text{H}$.Q8 A series circuit has 4Ω , 5Ω , 9Ω and 10Ω resistors. Which resistor has the most voltage across it? Justify your answer.Q9 Give the propagation constant of a symmetrical T-section and π -section.

Q10 Define transfer and driving point impedance of a 2-port network.

SECTION-B

- Q11 Determine frequency response in terms of resonant peak magnitude and corresponding frequency of a system having following closed loop transfer function : $C(s) = \frac{1}{s^2 + s + 1}$.
- Q12 Find the frequency at which a prototype T-section low-pass filter having cut-off frequency f_c have an attenuation of 15dB.
- Q13 Determine the current in the 5Ω resistor for the circuit shown using mesh analysis of Fig. 1.

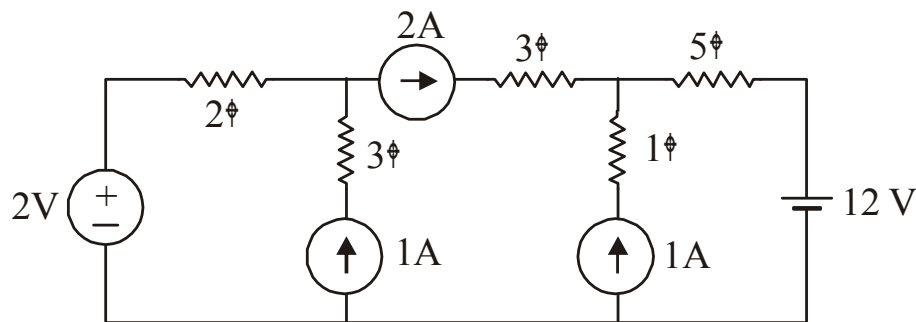


FIG.1

- Q14 In the circuit shown, S is moved from 1 to 2 at $t = 0$. Determine $i(t)$ and $v(t)$ for $t > 0$ through resistor if $i(0) = 2A$ of Fig. 2.

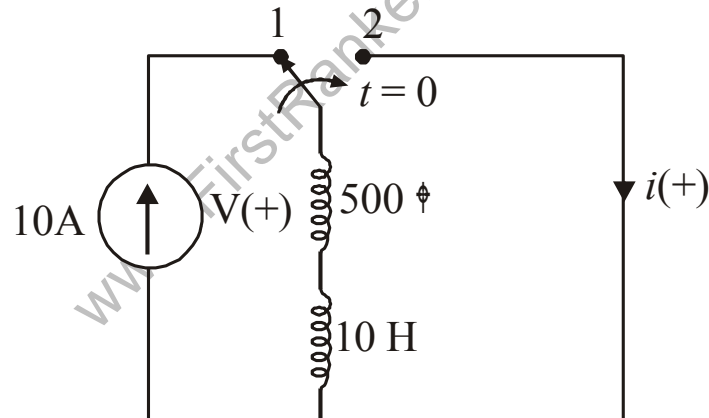


FIG.2

- Q15 State the necessary and sufficient conditions for a polynomial to be Hurwitz and Check whether $P(s) = s^4 + s^3 + 2s^2 + 4s + 1$ is Hurwitz or not.

SECTION-C

Q16 The driving point impedance is given by :

$$z(s) = \frac{(s+1)(s+4)}{(s)(s+2)(s+5)}$$

Obtain the Foster-I and Cauer-II forms.

Q17 Define all types of filters and draw their characteristics and block diagrams.

Q18 Find current I_L in the 5Ω resistor using Thevenin theorem and verify the result using Norton theorem of Fig. 3.

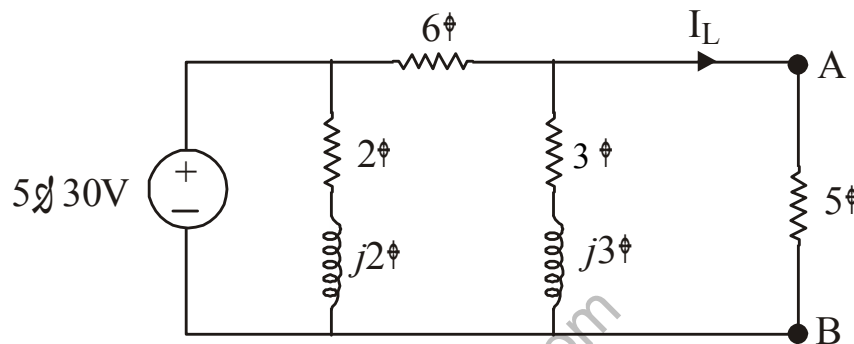


FIG.3

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.