

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 18

B.Tech. (Electrical & Electronics) (2018 Batch) (Sem.-4)

DIGITAL ELECTRONICS

Subject Code : BTEE-401-18

M.Code : 77606

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A**Write briefly :**

- Q1. Define Noise Margin?
- Q2. State the different classification of binary codes.
- Q3. State the commutative property of Boolean algebra.
- Q4. What is Propagation Delay?
- Q5. What is a Karnaugh Map?
- Q6. Give the comparison between synchronous & Asynchronous sequential circuits.
- Q7. State and prove De Morgan's theorem.
- Q8. Obtain the canonical sum of products of the function $Y = AB + ACD$.
- Q9. What is EEPROM?
- Q10. Which gates are called as the Universal Gates? What are its advantages?

SECTION-B

- Q11. Simplify the given expression $AB + (AC)' + AB'C (AB + C)$.
- Q12. Explain the flip-flop excitation tables for JK flip-flop.
- Q13. State the postulates and theorems of Boolean algebra.
- Q14. Design and explain a comparator to compare two identical words.
- Q15. Explain in detail about Race around condition.

SECTION-C

- Q16. Determine the prime implicants of the function
- $$F(W,X,Y,Z) = _ (1,4,6,7,8,9,10,11,15)$$
- Q17. Explain with neat diagrams TTL.
- Q18. Explain the working of BCD Ripple Counter with the help of state diagram and logic Diagram.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.