

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech. (EE) (2012 Onwards)/(Electrical & Electronics) (2011 Onwards)
B.Tech. (Electrical Engineering & Industrial Control)/(Electronics &
Electrical) (2012 to 2017)
(Sem.-3)

TRANSFORMERS AND DIRECT CURRENT MACHINES

Subject Code : BTEE-302

M.Code : 57093

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**Q1 Answer briefly :**

- a) Discuss the working principle of a single phase transformer.
- b) What do you mean by voltage regulation of a transformer?
- c) Write any two applications of an autotransformer.
- d) What are the reasons of higher efficiency of autotransformers as compared to conventional transformers?
- e) What are the possible connections for a 3 phase transformer bank?
- f) What is armature reaction?
- g) What are the different types of DC generators?
- h) What is critical field resistance of a DC shunt generator?
- i) Explain the working principle of a DC motor.
- j) Draw the equivalent circuit of a DC motor armature.

SECTION-B

- Q2 The maximum efficiency of a 100 KVA single phase transformer is 98% and occurs at 80% of full load at 0.8 power factor lagging. If the leakage impedance of the transformer is 5%, find the voltage regulation at full load.
- Q3 The primary and secondary voltages of an autotransformer are 500V and 400V respectively. Show with the help of a diagram the current distribution in the windings when the secondary current is 100 A. Also calculate the economy in the conductor material.
- Q4 Explain the short circuit and open circuit tests on a three winding transformer.
- Q5 Define Commutation. Explain the process of commutation in DC generators with neat sketches.
- Q6 Explain the principle of torque production in a DC motor. Also derive the torque equation for a DC motor

SECTION-C

- Q7 Define Transformer Efficiency and find out the condition for maximum efficiency. A single phase transformer working at unity power factor has an efficiency of 90% at both half load and at full load of 500 W. Determine the efficiency at 75% full load and the maximum efficiency.
- Q8 Derive the expression for finding out the EMF equation of a DC machine. An 8 pole lap connected armature has 40 slots with 12 conductors per slot generates a voltage of 500V. Determine the speed at which it is running if the flux per pole is 50 mWb.
- Q9 Discuss the different methods of speed control of a DC motor.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.