

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 18

B.Tech. (Electronics & Communication Engineering) (2018 Batch)
(Sem.-4)

ANALOG CIRCUITS
Subject Code : BTEC-401-18
M.Code : 77565

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**Write briefly :**

- Q1. Define trans-conductance and drain resistance with respect to JFET.
- Q2. Derive the relation between α and β with respect to BJT.
- Q3. Draw hybrid small signal model for a transistor in CE configuration.
- Q4. Draw the block diagram of Voltage Series feedback and Current Series feedback diagram.
- Q5. The voltage gain of an amplifier without feedback is 3000. Calculate the voltage gain of the amplifier if negative voltage feedback is introduced in the circuit. Given that feedback fraction $m_v = 0.01$.
- Q6. What is the difference between amplifier and oscillator?
- Q7. Write Barkhausen criterion for oscillators.
- Q8. Why power amplifiers are called large signal amplifiers?
- Q9. Explain the loading effect in amplifiers.
- Q10. What are the different coupling schemes used in multistage amplifiers?

SECTION-B

- Q11. Draw the high frequency model of a CE transistor and explain each component of it.
- Q12. Why does gain of amplifier falls off at low and high frequencies? Explain with an appropriate diagram.
- Q13. Describe the effect of feedback on gain and bandwidth.
- Q14. Explain the working of RC phase shift oscillator and derive for its frequency of Oscillation.
- Q15. What is harmonics distortion in power amplifier? Discuss the operation of a class B power amplifier and derive its maximum power conversion efficiency.

SECTION-C

- Q16. Draw and explain input and output characteristics of CB amplifier. Write any practical application of CB amplifier.
- Q17. Draw the circuit for Voltage shunt amplifier and justify the type of feedback. Derive the expressions for A_v , β , R_i and R_o for the circuit.
- Q18. Write short notes on the following :
- a) Clapp Oscillators
 - b) Cascade Amplifiers

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.