

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 08

M.Tech.(ECE) (Sem.-1)
ELECTRONICS SYSTEM DESIGN

Subject Code : EC-502

M.Code : 36203

Time : 3 Hrs.

Max. Marks : 100

INSTRUCTION TO CANDIDATES :

1. Attempt any FIVE questions out of EIGHT questions.
2. Each question carries TWENTY marks.

1. a) Implement the function $f = \sum m(0, 2, 3, 6, 7, 11) + \phi(1, 4, 8, 15)$ by using Q-M method. 10
b) Using the theorems minimize the following expression 10
$$F = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + ABC\overline{D}$$
2. a) Design and implement half and full subtractor using NOR gates. 12
b) Explain ROM and PLA. What is the difference between ROM and PLA? 8
3. a) Why shift registers are required? Discuss the various operation modes of shift registers. 10
b) List the design steps for next state decoders. 10
4. Design a circuit that will compare two 2-bit number. Implement the circuit using only NOR gates and then again repeat using only NAND gates? 20
5. a) What is a binary cell? Design a binary cell mentioning all appropriate design steps. 10
b) Define propagation delay? What is its significance? Also make a comparison between open collector and tri-state bus systems. 10
6. Implement the function $f = \sum m(0, 4, 6, 7, 9, 12, 14)$ using ROM, PLA and 4 : 1 multiplexer. 20





7. a) Explain the purpose of grounding and shielding in digital systems. 8
- b) What is tri-state logic circuit and how does it help building a tri-state bus system?
 Discuss the advantages of this logic in reducing hardware in system implementation. 12
8. Write short note on following : 20
- a) PAL
- b) Hazards
- c) Wired Logic

NOTE : Disclosure of identity by writing mobile number or making passing request on any page of Answer sheet will lead to UMC case against the Student.

