

www.FirstRanker.com

www.FirstRanker.com

Roll No. Total No. of Pages : 02 Total No. of Questions : 08 M.Tech.(ECE) (2016 Batch) (Sem1) ELECTRONICS SYSTEM DESIGN Subject Code : MTEC-101 M.Code : 74146					
Tim	ie : 3 Hrs.			Max. Marks:100	
INSTRUCTIONS TO CANDIDATES : 1. Attempt any FIVE questions in all. 2. Each question carry TWENTY marks.					
Q1	(a) Design a combinational circuit which can convert BCD code to E-3 code.				
	(b) With the help of 2:1 MUX generate the following function:				
	F (A, B, C, D) = $\Sigma$ (0, 3, 7, 8, 12, 13, 14)				
Q2.	2. Design combinational Circuit for following function using Q-M method.				
$F(A, B, C, D) = \Sigma (0,2,3,6,8,10,13,14,20,23,27,29) + d(11,12,22,24)$					
Q3. Design basic binary cell centred LM flip-flop specified by the following characteristic :					
		L	M	Qn	]
		0	0	Set	
		0	1	No Change	

Also define the excitation table.

J'

1

1

Q4. Only write the steps to design an asynchronous sequential machine and design a JK flip flop as an asynchronous machine.

Toggle

Reset

0

1

(S9)-1032

FirstRanker.com

www.FirstRanker.com

Q5. Write the advantages of MEV approaches to design an asynchronous machine and draw a circuit for

 $F(A,B,C,D) = \Sigma_m(1,2,3,5,6,8,1,1,12,13,14,15)$  using same approach.

- Q6. Write the advantages and disadvantages of PAL over PLA and design full sub-tractor using PLA and PAL, with neat diagrams.
- Q7. How the co-axial cable is interfaced with digital system explain with neat diagram.
- Q8. Explain any two :
  - (a) MSI decoder
  - (b) Timing and frequency consideration in controller design
  - (c) Tri state bus system.

www.FirstRanker.com

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.

**2** | M-74146

(S9)-1032