

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 08

M.Tech.(ECE) E-I (Sem.-2)
VLSI DESIGN
Subject Code : EC-511
M.Code : 36212
Time : 3 Hrs.
Max. Marks : 100
INSTRUCTIONS TO CANDIDATES :

1. Attempt any FIVE questions in all, out of EIGHT questions.
2. Each question carries TWENTY marks.

1.
 - a) Compare combination and sequential circuits with the help of examples. Also discuss the timing analysis of sequential circuits.
 - b) Explain Charge coupled devices with suitable diagrams.
2.
 - a) Reduce the following state table to a minimum number of states.

Present State	Next State		Present Output	
	X=0	1	X=0	1
a	h	c	1	0
b	c	d	0	1
c	h	b	0	0
d	f	h	0	0
e	c	f	0	1
f	f	g	0	0
g	g	c	1	0
h	a	c	1	0

- b) Realize the following state table using a minimum number of AND and OR gates together with a D flip-flop.

 $X_1X_2X_3$

	000	001	010	011	100	101	110	111	Z
A	A	A	B	B	B	B	A	A	0
B	A	B	B	A	A	B	B	A	1



3.
 - a) Tabulate the PAL programmable table and mark the fuse map in a PAL diagram for the BCD to Excess-3 code converter.
 - b) Discuss the structures of standard PLDs and complex PLDs in detail with suitable diagram.
4. Explain the basic Xilinx structure, configurable logic block and input/output block (IOB) of XC4000 family with the help of suitable diagrams.
5.
 - a) Explain the pre-defined and user-defined data types of VHDL language.
 - b) Explain pre-defined and user-defined attributes with the help of suitable examples.
6.
 - a) What is the need of hardware description language? Explain the design flow and basic terminology of VHDL language with suitable diagrams.
 - b) Write behavioural VHDL description for the 3-bit magnitude comparator.
7.
 - a) Explain various loop statements in Verilog.
 - b) Write the Verilog description of 4-bit ripple carry adder.
8. Write short notes on the following (any **TWO**) :
 - a) SRAM
 - b) Operators in VHDL
 - c) Tasks and functions in Verilog

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.

