

Roll No. 

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 01

Total No. of Questions : 08

**M.Tech. (EE) EI-II (2018 Batch) (Sem.-1)**  
**PWM CONVERTER AND APPLICATIONS**  
**Subject Code : MTEE-104A-18**  
**M.Code : 75221**

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. Attempt any FIVE questions out of EIGHT questions.
2. Each question carries TWELVE marks.

1. What are major differences between voltage and current source converters? Explain the working of a current source converter using circuit diagram and corresponding waveforms.
2. Classify different types of DC/AC converters. Draw neat circuit diagram of each type of these converters.
3. Discuss in detail space vector based PWM technique for bridge converters.
4. How a practical power electronic device behaves differently from that of ideal one? Explain how conduction losses are calculated in practical power electronic circuits?
5. A 3-phase, Y-connected, 60 Hz, 4-pole induction motor has the following parameters:  
 $R_1 = R_2 = 0.024\Omega$  and  $X_1 = X_2 = 0.12\Omega$ . The motor is controlled by the variable frequency control with a constant (V/f) ratio. For an operating frequency of 12Hz, calculate the maximum torque as a ratio of its value at the rated frequency for both motoring and braking.
6. Explain how current ripples are estimated in inverted fed drives?
7. With the help of a neat circuit diagram explain how switching converters are used for reactive power compensation.
8. Write short notes on :
  - a) Multilevel inverters
  - b) Bus clamping PWM

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**

