

Roll No. 

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 01

Total No. of Questions : 08

**M.Tech.(Power System) (Sem.-2)****H.V.D.C. TRANSMISSION****Subject Code : PEE-508****M.Code : 38810****Time : 3 Hrs.****Max. Marks : 100****INSTRUCTION TO CANDIDATES :**

1. Attempt any FIVE questions out of EIGHT questions.
2. Each question carries TWENTY marks.

- Q1 a) Explain the H.V.D.C. Power flow mechanism in details with all components. (12)  
b) Differentiate between H.V.D.C and EHVAC power flow link. (8)
- Q2. Draw and explain the working of 3-phase 6-pulse bridge converter with suitable diagrams, waveforms and applications. (20)
- Q3. a) What are difference between operating features of rectifier and inverter? (10)  
b) What are the roles of CIA and CEA and CC in HVDC? (10)
- Q4. a) Why reactive power compensation is required in HVDC substation? Explain them. (10)  
b) Explain static VAR system for the load compensation. (10)
- Q5. a) How harmonics is eliminated in HVDC? Explain. (5)  
b) Design a harmonic filter to reduce the telephone interface for HVDC. (15)
- Q6. Discuss and analyze the stability aspect of asynchronous link. (20)
- Q7. What is multi-terminal HVDC substations system? Explain with suitable diagram wave form analysis. (20)
- Q8. Write short notes on :  
a) Equivalent circuit of HVDC line. (5)  
b) Protection of HVDC system. (5)  
c) Role of converter and inverter in HVDC. (5)  
d) Synchronous link stability. (5)

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**

