

FACULTY OF SCIENCE**B.Sc. (CBCS) V – Semester Examination, November / December 2019****SUBJECT : ELECTRONICS
(DSC) Paper - V
(Digital Electronics)****Time : 3 Hours****Max Marks : 60****PART – A (5x3 = 15 Marks)
(Short Answer Type)****Note : All the following FIVE question.**

1. Find the decimal equivalent of binary number 1111
2. Explain the working of AND gate with its circuit diagram and truth table.
3. Prove the Boolean identity $(A + B)(A + C) = A + BC$
4. Explain the operation of a decoder
5. Explain working of R-S flip flop with diagrams and truth table.
6. Explain Ring Counter.
7. Explain the working of synchronous counter.
8. Differentiate between static and dynamic RAM.

**PART – B (45 Marks)
(Essay Answer Type)****Note : All the following three question.**

9. a. What is 2's complement of binary number? Explain the subtraction of binary numbers using 2's complement method. 11

OR

- b. Draw the circuit diagram of Half adder and Full adder and give their truth tables.

10. a. Write and prove the De-Morgan theorems. 11

OR

- b. Draw the circuit diagram of De-multiplexer and discuss its operation with help of truth tables

11. a. Describe the working of Master Slave JK flip flop with neat circuit diagram. 11

OR

- b. Explain Universal shift register using IC 7496.

12. a. State the difference between ROM, PROM and EPROM. 12

OR

- b. Explain working of ripple counter (IC7493) with truth table and timing diagrams.