

www.FirstRanker.com www.FirstRanker.com  
**GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER– III (New) EXAMINATION – WINTER 2019**

**Subject Code: 3131103**

**Date: 3/12/2019**

**Subject Name: Network Theory**

**Time: 02:30 PM TO 05:00 PM**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

|            |  | Marks     |
|------------|--|-----------|
| <b>Q.1</b> | (a) Draw Ideal and Practical Current and Voltage source characteristics. In what respect practical current and voltage sources are different from ideal current and voltage sources.   | <b>03</b> |
|            | (b) Derive current, voltage, power and energy equations of two terminal elements Resistor, Inductor and Capacitor.   | <b>04</b> |
|            | (c) Determine the current in $4\Omega$ resistor using mesh analysis for the network shown in figure 1.   | <b>07</b> |
| <b>Q.2</b> | (a) Derive the conduction of maximum power transfer for the variable resistance as a load circuit.   | <b>03</b> |
|            | (b) What is equivalent circuit of the charged and uncharged inductor and capacitor at $t=0+$ and $t=\infty$ .  | <b>04</b> |
|            | (c) Determine the value of $I_1$ using superposition theorem for the circuit shown in figure 2.  | <b>07</b> |
|            | <b>OR</b>  |           |
|            | (c) Find the current in $4\Omega$ resistor for the circuit shown in figure 3 using Thevenin's theorem and also find maximum power dissipation by the $4\Omega$ .   | <b>07</b> |
| <b>Q.3</b> | (a) Define the time-constant of RL and RC networks and explain the significance of the time-constant.  | <b>03</b> |
|            | (b) In the network shown in figure 4, the switch k is moved from position 1 to 2 at $t=0$ , steady state having previously been attained. Determine the current $i(t)$ for the $t \geq 0$ .  | <b>04</b> |
|            | (c) In the network shown in figure 5, the switch k is changed from position 1 to 2 at $t=0$ . Find values of $i$ , $di/dt$ and $d^2i/dt^2$ at $t=0+$ if $R=1000\Omega$ , $L=1H$ , $C=0.1\mu F$ and $V=100V$ .  | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.3</b> | (a) In the network shown in figure 6, the switch k is closed at $t=0$ , a steady state having previously been attained. Find $i(t)$ for $t \geq 0$ .   | <b>03</b> |
|            | (b) An exponential voltage $v(t)=4e^{-3t}$ is applied at time $t=0$ to a series R-L circuit consisting of a resistor $R=0.5\Omega$ and inductor $L=0.25H$ as shown in figure 7 Obtain the expression of current $i(t)$ for $t \geq 0$ . Assume zero current through the inductor before switching. | <b>04</b> |
|            | (c) Obtain z-parameters for the network shown in figure 8.   | <b>07</b> |
| <b>Q.4</b> | (a) Write the procedure to obtain Thevenin's equivalent voltage and resistance for the different types of network.   | <b>03</b> |
|            | (b) In the network shown in figure 9 the switch k is moved from position a to b at $t=0$ , a steady state existing in  | <b>04</b> |

- position a before  $t=0$ . Solve for the current  $i(t)$  using the Laplace transformation method. www.FirstRanker.com 07
- (c) Find the Norton's equivalent circuit for the network shown in figure 10 and obtain current in  $10\Omega$  (load resistor). www.FirstRanker.com 07

**OR**

- Q.4** (a) Find the Laplace transform of the signal  $f(t)=e^{-at}\sin(wt)$ . 03
- (b) Obtain the voltage across the capacitor in the LC circuit shown in figure 11 using Laplace transformation technique, if initial voltage across capacitor is 2V. 04
- (c) Using nodal analysis determine the current  $I$  in the circuit shown in figure 12. 07
- Q.5** (a) Define (1) Oriented Graph (2) Tree and (3) Incidence matrix. 03
- (b) Define symmetry and reciprocity conditions for two port network also derive conditions of symmetry and reciprocity of the two port network in terms of  $Z$  parameters. 04
- (c) For the circuit shown in figure 13 draw the oriented graph and obtain the (1) Incidence matrix (2) f-cutset matrix and (3) tieset matrix. 07

**OR**

- Q.5** (a) List out the necessary and sufficient conditions for positive real function. 03
- (b) Determine the inductance between the terminals for three coil shown in figure 14. 04
- (c) For the circuit shown in figure 15 draw the oriented graph and obtain the (1) Incidence matrix (2) f-cutset matrix and (3) tieset matrix. 07

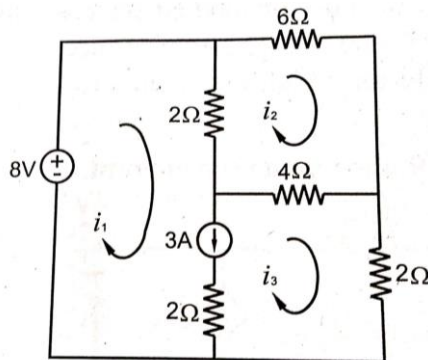


Figure 1

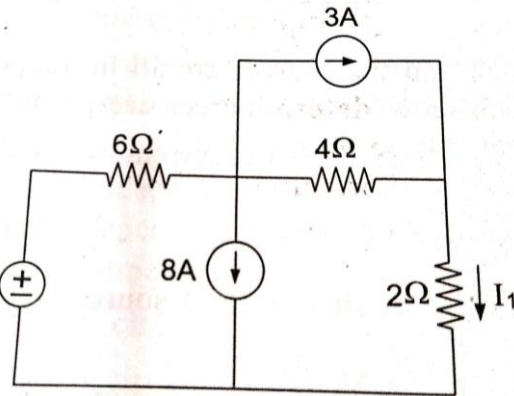


Figure 2

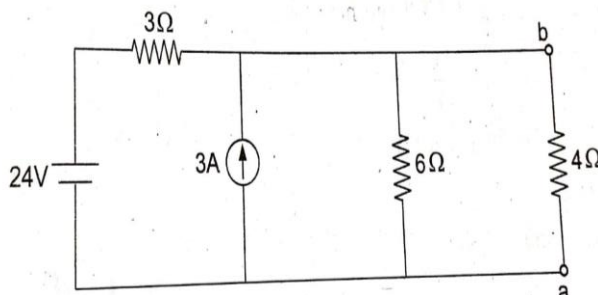


Figure 3

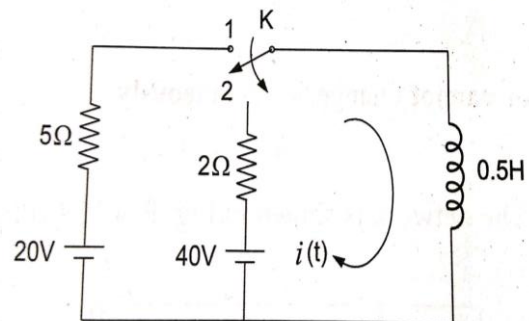


Figure 4

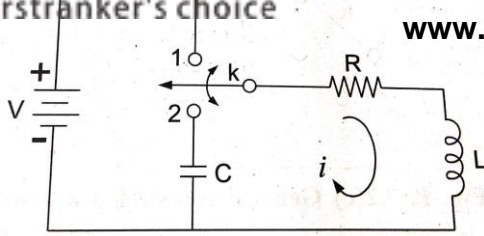


Figure 5

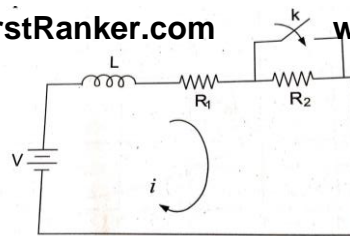


Figure 6

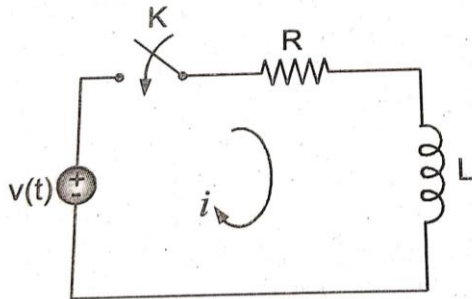


Figure 7

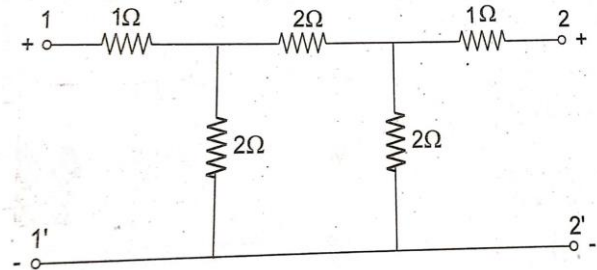


Figure 8

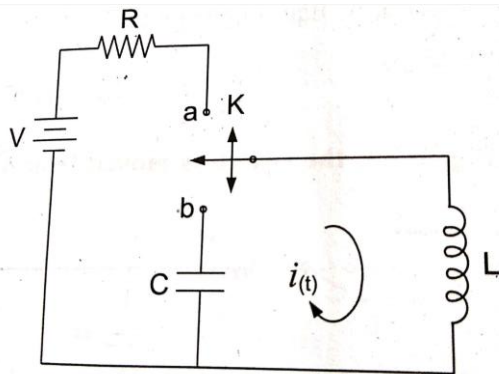


Figure 9

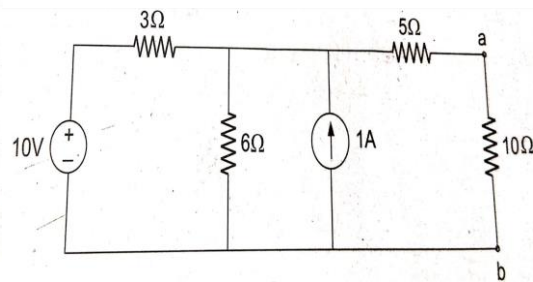


Figure 10

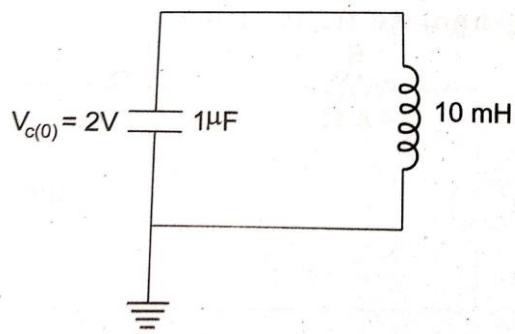


Figure 11

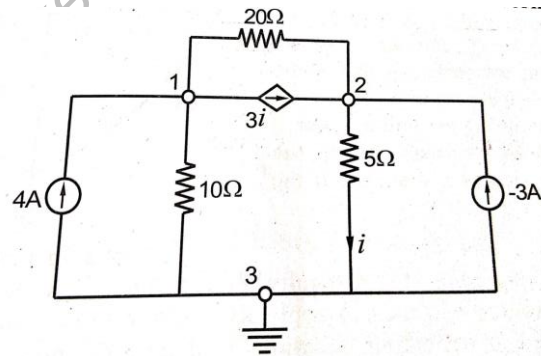


Figure 12

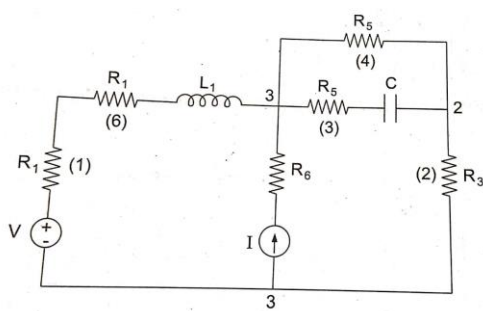


Figure 13

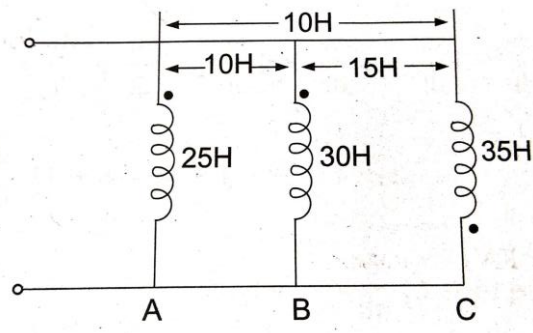


Figure 14

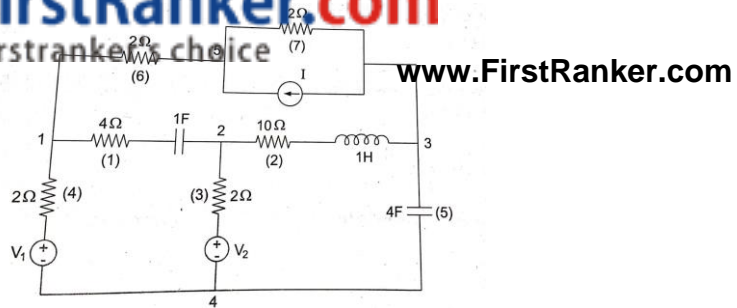


Figure 15

\*\*\*\*\*

www.FirstRanker.com