

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER– III (New) EXAMINATION – WINTER 2019

Subject Code: 3131704

Date: 26/11/2019


Subject Name: Digital Electronics

Time: 02:30 PM TO 05:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
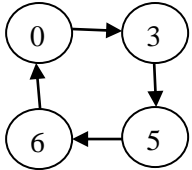
| | | MARKS |
|------------|---|-----------|
| Q.1 | (a) Give the comparison of 1's and 2's complements. | 03 |
| | (b) Explain De Morgan's theorem with suitable example. | 04 |
| | (c) Explain the commutative law, associative law, and distributive law in Boolean algebra with example | 07 |
| Q.2 | (a) Convert $(163.875)_{10}$ to binary. | 03 |
| | (b) Design Full Adder using two Half Adder and one two input OR gate. | 04 |
| | (c) Implement the following function with 8:1 multiplexer: $F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$ | 07 |
| | OR | |
| | (c) Explain the working of 4:1 multiplexer. | 07 |
| Q.3 | (a) What do you mean by universal gates? Implement NOT, AND, OR with any one universal gate. | 03 |
| | (b) Implement 4 bit Shift Register for 1010 binary pattern. | 04 |
| | (c) A combinational circuit is defined by functions: $F_1(A, B, C) = \sum m(3, 5, 6, 7)$ $F_2(A, B, C) = \sum m(0, 2, 4, 7)$ Implement the circuit with PLA having three inputs, four product terms and two outputs. | 07 |
| | OR | |
| Q.3 | (a) Explain the operation of master slave J-K flip flop. | 03 |
| | (b) Explain gray code in detail. | 04 |
| | (c) Design a type T counter for given state diagram | 07 |
| |  | |
| Q.4 | (a) Describe Fan In, Noise Margin and Propagation Delay parameters for digital IC. | 03 |
| | (b) Explain ROM with block diagram. Give classification of ROM. | 04 |
| | (c) Design 3 to 8 line decoder with neat sketch and truth table. | 07 |
| | OR | |
| Q.4 | (a) Simplify Boolean function $F = A'B'C' + B'CD' + A'BCD' + AB'C'$ using K map. | 03 |
| | (b) Explain TTL gate with Totem pole output. | 04 |

- (e) Explain 4 bit magnitude comparator with necessary Boolean expression. **07**
- Q.5** (a) Explain D flip-flop. **03**
 (b) Explain arithmetic ,logic micro operation. **04**
 (c) Minimize the following function using tabulation method: **07**
 $F(w, x, y, z) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$
- OR**
- Q.5** (a) Design full subtracter with necessary derivation of functions. **03**
 (b) Explain the following register transfer operation with the help of necessary diagram **04**
 $T1: C \leftarrow A$
 $T2: C \leftarrow B$
 Assume A, B and C are 4 – bit registers.
- (c) Simplify the Boolean expression $F(A,B,C,D) = \sum(2,3,6,7,8,10,11,13,14)$ using K Map. **07**
