<b>First</b>	tRa	inker.com	
Firstran	ker's	GUIARAT TEGHNOTOGIGAI UNIVERSITA	er.com
		BE - SEMESTER- III (New) EXAMINATION – WINTER 2019	
Subje	Subject Code: 3131706 Date: 30/1		
Subje	ct Na	me: Measurement and Instruments	
Time:	02:3	0 PM TO 05:00 PM Total Mar	:ks: 70
Instruct	tions:	ttempt all questions	
	1. Au 2. M	ake suitable assumptions wherever necessary.	
	3. Fi	gures to the right indicate full marks.	
0.1		Demonstrate Indianting terms instances	Marks
Q.1	(a) (b)	Compare: Accuracy and Precision with example	03 04
	$(\mathbf{D})$	Explain Loading affact and its elimination in AC and DC Maters	07
	(C)	Explain Loading effect and its eminiation in AC and DC Meters.	07
Q.2	(a)	What is transformer? Write down types and application of	03
	(h)	Explain frequency measurement using Zero beat frequency meter	04
	(c)	Explain working principle of PMMC meter in detail with its neat	07
		diagram.	
		OR	~-
0.1	(c)	Explain Digital multimeter with its block diagram.	07
Q.3	(a) (b)	Obtain Lissaious pattern using CRO in X-V mode for frequency	03
	(0)	measurement of 2:1, 3:1, 3:2 & 4:1 with its procedure & Waveform.	04
	(c)	Explain block diagram of CRO with function of each block in	07
		details.	
0.2	$(\mathbf{a})$	OR Identify different techniques for measurement of medium registeres	02
Q.3	(a)	Explain any one in detail	03
	<b>(b)</b>	Find resistance values for Ayrton shunt to provide an ammeter with	04
		current ranges of 1 A, 5 A and 10 A, A basic PMMC meter with an	
		internal resistance of 50 Ohm and a full scale deflection current of 1	
	(e)	mA is to be used Explain Kalvin double bridge for low resistance measurement with	07
	(C)	neat diagram	07
Q.4	<b>(a)</b>	Explain Electronic Timers.	03
	<b>(b)</b>	Explain Hay's bridge method to measure unknown Inductance.	04
	(c)	Explain Schering bridge method to measure unknown capacitance	07
		with its circuit diagram and calculations.	
04	(9)	Explain Distortion Analyzer with example	03
2	(b)	Explain Sweep frequency generator.	03
	(c)	Explain Universal Timer-Counter with its block diagram.	07
Q.5	<b>(a)</b>	Explain Conductive coupling interference with example.	03
	<b>(b)</b>	What is Inductive Interference? Explain How it can be reduced.	04
	(c)	What is Current transformer? Explain its working with construction	07
		OR	
Q.5	<b>(a)</b>	Explain Ground level interference in brief.	03
	<b>(b)</b>	Explain Power factor measurement using Analog meter.	04
	(c)	Explain 3 – Phase Power measurement using 2 watt meter method	07
		with necessary magrains.	

1

\*\*\*\*\*