

# GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (Old) EXAMINATION – WINTER 2019

**Subject Code: 131101**
**Date: 30/11/2019**
**Subject Name: Basic Electronics**
**Time: 02:30 PM TO 05:00 PM**
**Total Marks: 70**
**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a) Answer the following questions: 07**
- 1) Sketch the piecewise linear characteristics of PN junction diode.
  - 2) What is cut-in voltage? Write approx. value of cut-in voltage for silicon and germanium diode.
  - 3) Define Thermal resistance.
  - 4) Define Mean life time of a carrier.
  - 5) What do you mean by PIV (Peak Inverse voltage)? Enlist the value of PIV for different rectifiers.
  - 6) What is depletion region in PN junction diode.
  - 7) Explain Zener breakdown phenomena.
- (b) Explain the Hall effect and obtain the expression of Hall coefficient. List the applications of Hall effect. 07**
- Q.2 (a) Draw and explain bridge rectifier circuit with capacitor filter. Draw necessary waveforms. 07**
- (b) The resistivity of intrinsic silicon is  $3 \times 10^5 \Omega\text{-cm}$  at  $30^\circ\text{C}$ . Calculate the intrinsic concentration at  $100^\circ\text{C}$ . Assume  $\mu_n = 0.13 \text{m}^2/\text{V-sec}$  and  $\mu_p = 0.05 \text{m}^2/\text{V-sec}$  at  $30^\circ\text{C}$ . 07**
- OR**
- (b) A silicon sample is non-uniformly doped with donor impurity of  $10^{14} \text{m}^{-3}$ . A current density of  $10 \text{mA/cm}^2$  is generated when electric field of  $3 \text{V/cm}$  is applied across it. Find the concentration gradient at  $27^\circ\text{C}$ . Given:  $\mu_n = 1500 \text{cm}^2/\text{V-sec}$ . 07**
- Q.3 (a) Draw the circuit of Common Emitter configuration of transistor. Explain input and output characteristics. Also derive  $\alpha = \beta / \beta + 1$ . 07**
- (b) For the circuit shown in Figure (1), explain working of the circuit and draw output waveform for given input signal. Also draw transfer characteristics. 07**
- OR**
- Q.3 (a) What is biasing? Why biasing is required for transistor? List biasing methods for transistor. Draw and explain the circuit of voltage divider biasing 07**
- (b) The silicon transistor used in the circuit of Figure (2) has  $V_{CE(\text{sat})} = 0.2 \text{V}$ ,  $V_{BE(\text{sat})} = 0.8 \text{V}$ ,  $V_{BE(\text{active})} = 0.7 \text{V}$ ,  $V_{BE(\text{cut in})} = 0.5 \text{V}$  and  $\beta = 100$ . (I) Show that the transistor is in saturation. (II) Calculate the value of  $R_E$  for which the transistor just comes out of saturation. 07**
- Q.4 (a) Define stabilization factors;  $S$ ,  $S'$ , and  $S''$ . Also derive expressions for  $S$  and  $S'$  for self bias transistor circuit. 07**
- (b) The transistor used in the circuit of Figure (3) has the following parameters:  $h_{ie} = 500 \Omega$ ,  $h_{re} = 2.4 \times 10^{-4}$ ,  $h_{fe} = 60$  and  $h_{oe} = 1/40 \text{k}$ . Calculate : [1]  $V_o/V_S$  [2]  $R'_i$  [3]  $R'_o$ . Assume all capacitors to be very large. 07**
- OR**
- Q.4 (a) Draw circuit of an idealized class B push pull power amplifier and explain its operation with the help of necessary waveforms. 07**
- (b) Calculate the dc bias voltages and currents for the circuit shown in Figure (4). 07**

- Q.5 (a) Derive expressions for  $A_v$ ,  $R_i$ ,  $A_{v_s}$  and  $V_o$  in terms of CE h-parameters for emitter follower circuit. **07**
- (b) Draw and explain working of diode compensation circuit for  $V_{BE}$  for self-stabilization in amplifier circuit. **07**

OR

- Q.5 (a) Draw structure of n-channel JFET and explain its working. **07**
- (b) Draw a structure of p-channel MOSFET. Explain its working for enhancement type. Also draw and explain drain characteristics and transfer curve for the same device. **07**

\*\*\*\*\*

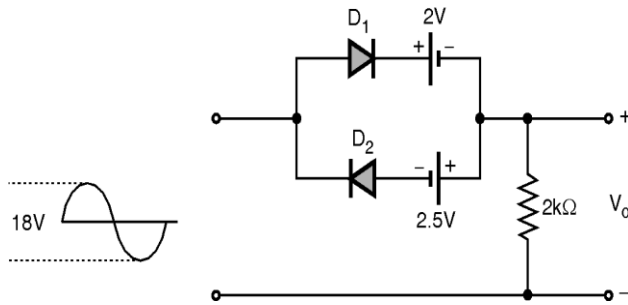


Figure (1)

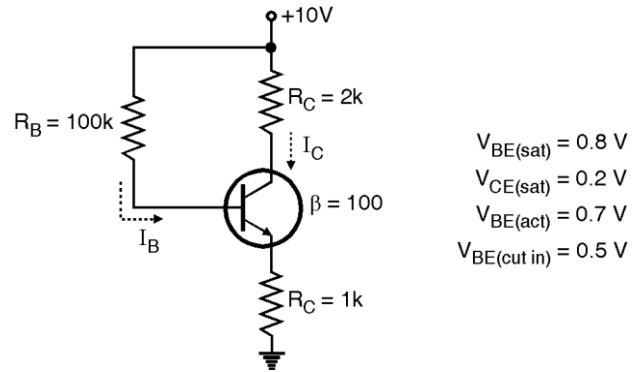


Figure (2)

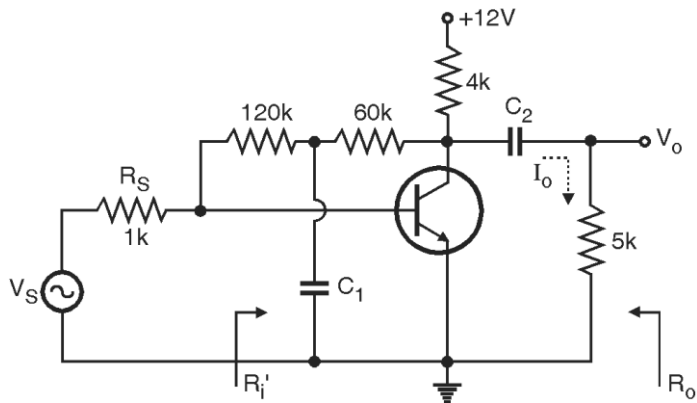


Figure (3)

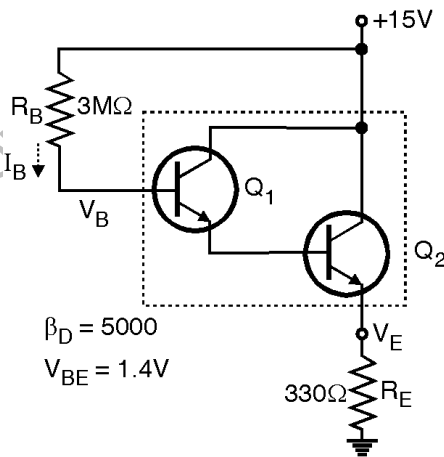


Figure (4)