

**GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER- IV (New) EXAMINATION – WINTER 2019**

**Subject Code: 2141706**

**Date: 14/12/2019**

**Subject Name: Analog Signal Processing**


**Time: 10:30 AM TO 01:00 PM**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

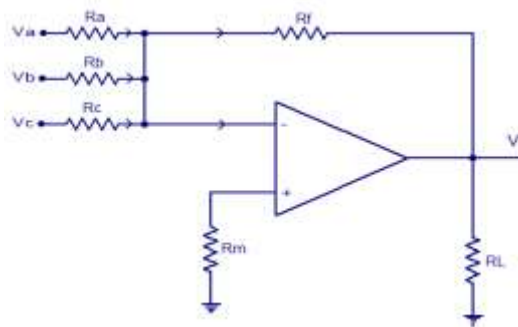- Q.1** (a) Draw the pin diagram of op-amp 741 and explain the function of each pin. **03**  
 (b) Define the following terms: **04**  
 (i) Common mode rejection ratio (ii) Slew Rate  
 (iii) Supply voltage rejection ratio (iv) Input offset voltage  
 (c) Draw and explain the Voltage series feedback amplifier (Non-inverting amplifier with feedback), also derive the equation of close loop voltage gain. **07**
- Q.2** (a) Draw and explain the Unity Gain Amplifier. **03**  
 (b) If  $R_a = R_b = R_c = R_m = 2\text{k}\Omega$ ,  $R_f = 3\text{ k}\Omega$ ,  $R_L = 5\text{ k}\Omega$ ,  $V_a = 0.75\text{v}$ ,  $V_b = 1\text{v}$  and  $V_c = 1.25\text{v}$ , Find the value of  $V_o$ . **04**



- (c) Write short note on RC phase shift Oscillator. **07**  
**OR**  
 (c) Write a short note on Wien Bridge oscillator. **07**
- Q.3** (a) Draw and explain the V-I converter circuit with floating load. **03**  
 (b) Draw and explain the Schmitt trigger circuit with the help of op-amp. **04**  
 (c) Explain differentiator circuit using op-amp in detail. **07**  
**OR**
- Q.3** (a) Enlist six ideal characteristics of op-amp 741. **03**  
 (b) Short note: Sub-tractor amplifier using op amp. **04**  
 (c) Explain integrator circuit using op-amp in detail. **07**
- Q.4** (a) Draw and explain the Averaging amplifier. **03**  
 (b) Describe the working of Zero crossing detector. **04**  
 (c) Draw and explain the Successive Approximation type ADC. **07**  
**OR**
- Q.4** (a) Draw and explain the circuit diagram of the Negative Clipper. **03**  
 (b) Write a short note on instrumentation amplifier using three op-amps. **04**  
 (c) Explain in detail the binary weighted register type D/A converter. **07**
- Q.5** (a) Explain all - pass filter with necessary diagrams. **03**  
 (b) Draw and explain the circuit diagram of the Positive Clamper. **04**

- (c) Explain the monostable multivibrator using 555 timer with its internal block diagram and its timing waveforms. **07**

**OR**

- Q.5** (a) Explain band-pass filter with necessary diagrams. **03**  
(b) Draw and explain the offset voltage compensating network for non-inverting amplifier. **04**  
(c) Explain the astable multivibrator using 555 timer with its internal block diagram and its timing waveforms. **07**

\*\*\*\*\*

www.FirstRanker.com