

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– I & II (OLD) EXAMINATION – WINTER 2019****Subject Code: 110005****Date: 11/01/2020****Subject Name: Elements Of Electrical Engineering****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Define the following terms with respect to AC waveforms: **07**  
(1) Angular velocity (2) Form factor (3) Crest Factor (4) Instantaneous Value  
(5) RMS Value (6) Phase angle (7) Frequency
- (b) Compare electric circuit and magnetic circuit by their similarities and dissimilarities. **07**
- Q.2** (a) Define the following terms with reference to Electrostatics & Electromagnetic: **07**  
(1) Electric potential (2) Electric flux density (3) Permittivity (4) Electric field intensity (5) MMF (6) Magnetic flux density (7) Reluctance
- (b) A 100 V, 100 W lamp is connected in series with 100 V, 60 W lamp across 200 V supply. Determine current drawn and power consumed by each lamp. **07**
- Q.3** (a) Explain resonance in series R-L-C circuit with graphical representation and resonance curve. **07**
- (b) Explain the method of transforming a star network into a delta network. **07**
- Q.4** (a) Explain two wattmeter method for power measurement in 3-phase delta connected load. **07**
- (b) Derive an expression for the energy stored in an inductor of self inductance 'L' henrys carrying the current of 'I' amperes. **07**
- Q.5** (a) A circuit consists of a pure inductor, a pure resistor and a capacitor connected in series. When the circuit is supplied with 100 V, 50 Hz supply, the voltage across inductor and resistor are 240 V and 90 V respectively. If the circuit takes 10 A leading current, calculate (i) value of inductance, resistance and capacitance (ii) power factor of the circuit (iii) voltage across capacitor. **07**
- (b) Derive expressions of voltage and current for capacitor of C farads during charging process. **07**
- Q.6** (a) Explain the construction of a cable with functions of its various parts with the help of neat diagram. **07**
- (b) Explain charging and discharging of Lead acid battery. **07**
- Q.7** (a) What is importance of earthing ? Explain plate earthing with diagram. **07**
- (b) Explain the types of lighting schemes with suitable diagrams. **07**

\*\*\*\*\*